



BENHA UNIVERSITY  
FACULTY OF ENGINEERING AT SHOUBRA

**ECE-312**  
**Electronic Circuits (A)**

Lecture #4  
BJT Modeling and  $r_e$  Transistor  
Model (small signal analysis)

**Instructor:**  
**Dr. Ahmad El-Banna**

OCTOBER 2014



# Remember !

## Lectures List

Week#1

- Lec#1: **Introduction and Basic Concepts**

Week#2

- Lec#2: **BJT Review**
- Lec#3: **BJT Biasing Circuits**

Week#3

- Lec#4: **BJT Modeling and  $r_e$  Transistor Model**
- Lec#5: **Hybrid Equivalent Model**

Week#4

- Lec#6: **BJT Small-Signal Analysis**
- Lec#7: **Systems Approach**

Week#5

- Lec#8: **General Frequency Considerations**
- Lec#9: **BJT Low Frequency Response**

Week#6

- Lec#10: **BJT High Frequency Response**
- Lec#11: **Multistage Frequency Effects and Square-Wave Testing**

( 2 )



# Remember !

## Lectures List

Week#1

- Lec#1: Introduction and Basic Concepts

Week#2

- Lec#2: BJT Review
- Lec#3: BJT Biasing Circuits

Week#3

- Lec#4: BJT Modeling and  $r_e$  Transistor Model
- Lec#5: Hybrid Equivalent Model

Merged in  
two lectures  
only ☺

Week#4

- Lec#6: BJT Small-Signal Analysis
- Lec#7: Systems Approach

Week#5

- Lec#6: General Frequency Considerations
- Lec#7: BJT Low Frequency Response

Week#6

- Lec#8: BJT High Frequency Response
- Lec#9: Multistage Frequency Effects and Square-Wave Testing

3



# Agenda

Amplification in the AC Domain

BJT transistor Modeling

The  $r_e$  Transistor Model (small signal analysis)

Effect of  $R_L$  and  $R_s$  (System approach)

Determining the Current Gain

Summary Table

( 5 )


# AMPLIFICATION IN THE AC DOMAIN



# Amplification in the AC Domain


$\eta = P_o/P_i$  cannot be greater than 1.

In fact, a *conversion efficiency* is defined by  $\eta = P_{o(\text{ac})}/P_{i(\text{dc})}$ , where  $P_{o(\text{ac})}$  is the ac power to the load and  $P_{i(\text{dc})}$  is the dc power supplied.

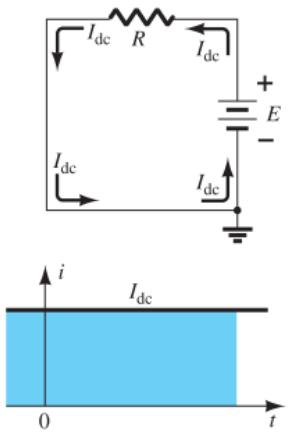

**FIG. 5.1**

Steady current established by a dc supply.

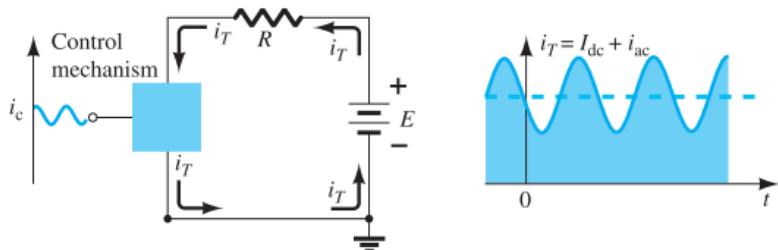

**FIG. 5.2**

Effect of a control element on the steady-state flow of the electrical system of Fig. 5.1.

- The superposition theorem is applicable for the analysis and design of the dc and ac components of a BJT network, permitting the separation of the analysis of the dc and ac responses of the system.







# BJT TRANSISTOR MODELING
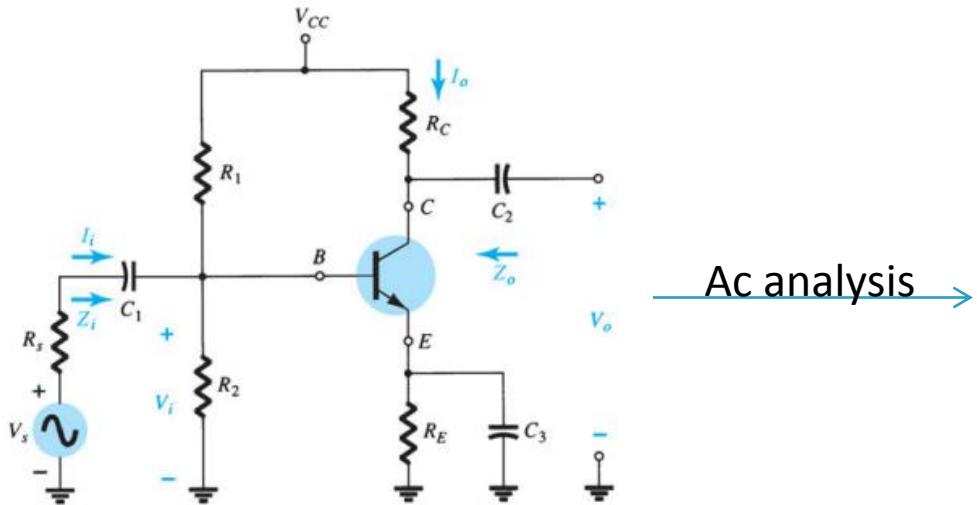
# BJT Transistor Modeling



- A **model** is a combination of circuit elements, properly chosen, that best approximates the actual behavior of a semiconductor device under specific operating conditions.



Ac analysis


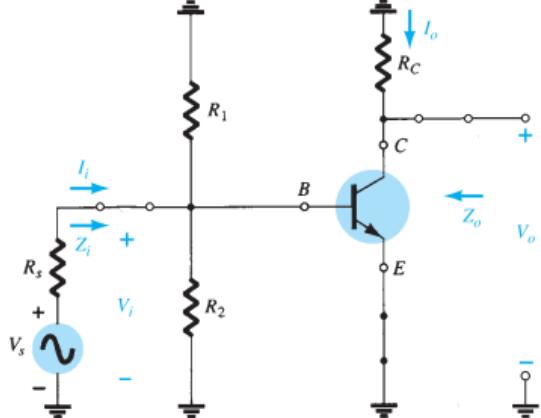


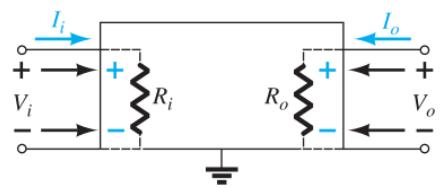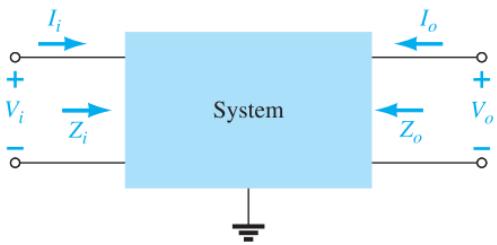- Defining the important parameters of any system.


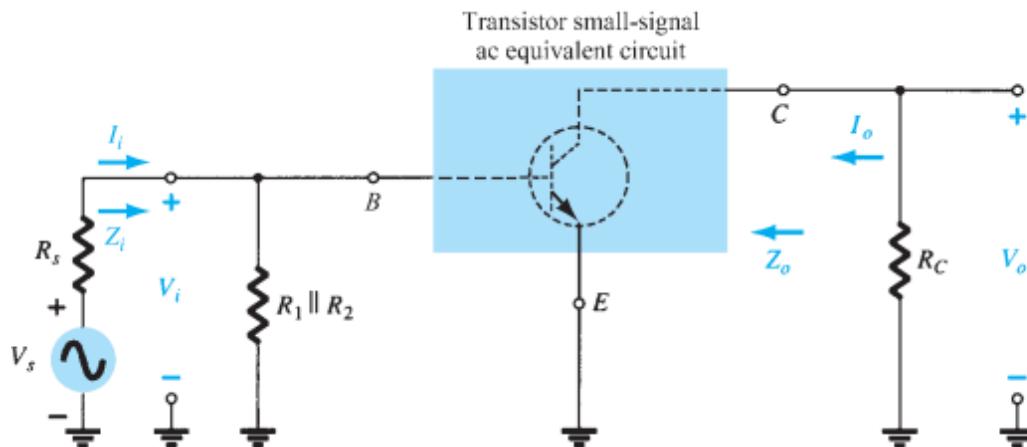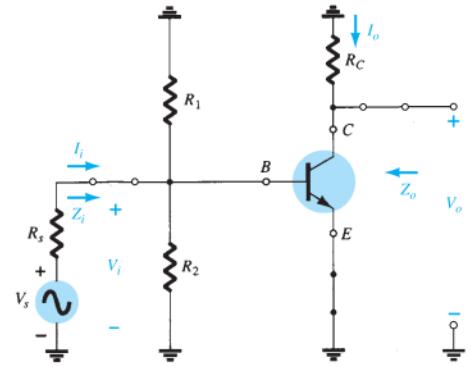
# BJT Transistor Modeling

- the ac equivalent of a transistor network is obtained by:
  - Setting all dc sources to zero and replacing them by a short-circuit equivalent
  - Replacing all capacitors by a short-circuit equivalent
  - Removing all elements bypassed by the short-circuit equivalents introduced by steps 1 and 2
  - Redrawing the network in a more convenient and logical form



( 9 )



( 10 )



- Common Emitter Configuration
- Common Base Configuration
- Common Collector Configuration
- $r_e$  Model in Different Bias Circuits

# THE $r_e$ TRANSISTOR MODEL

# The $r_e$ Transistor Model (CE)

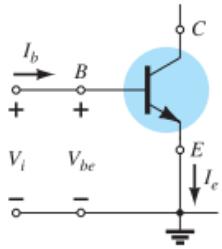


FIG. 5.8

Finding the input equivalent circuit for a BJT transistor.

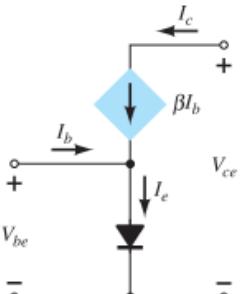


FIG. 5.12

BJT equivalent circuit.

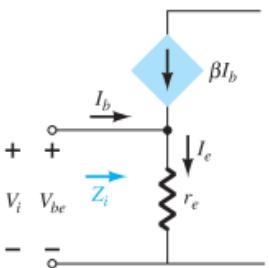


FIG. 5.13

Defining the level of  $Z_i$ .

$$\begin{aligned} Z_i &= \frac{V_i}{I_b} = \frac{V_{be}}{I_b} \\ V_{be} &= I_e r_e = (I_c + I_b)r_e = (\beta I_b + I_b)r_e \\ &= (\beta + 1)I_b r_e \\ Z_i &= \frac{V_{be}}{I_b} = \frac{(\beta + 1)I_b r_e}{I_b} \end{aligned}$$

$$Z_i = (\beta + 1)r_e \cong \beta r_e$$

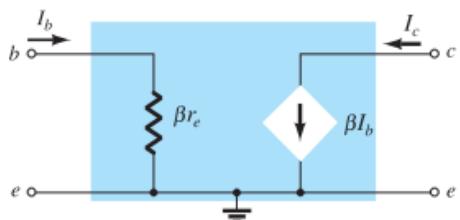


FIG. 5.14

Improved BJT equivalent circuit.

## Early Voltage

$$r_o = \frac{\Delta V}{\Delta I} = \frac{V_A + V_{CEQ}}{I_{CQ}}$$

$$r_o \cong \frac{V_A}{I_{CQ}}$$

$$\text{Slope} = \frac{\Delta y}{\Delta x} = \frac{\Delta I_C}{\Delta V_{CE}} = \frac{1}{r_o}$$

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C}$$

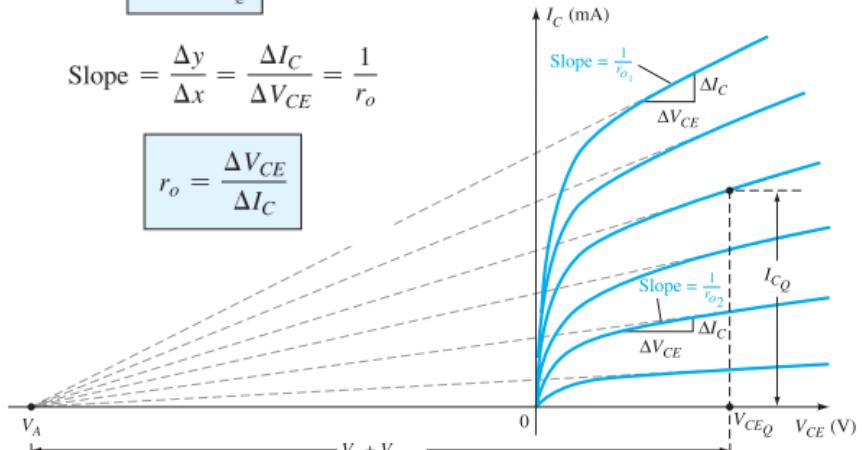


FIG. 5.15  
Defining the Early voltage and the output impedance of a transistor.


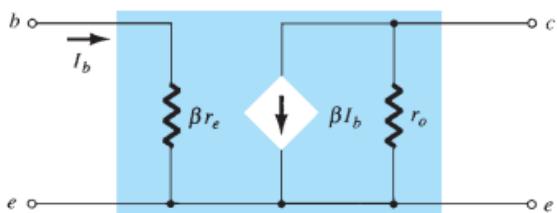


FIG. 5.16

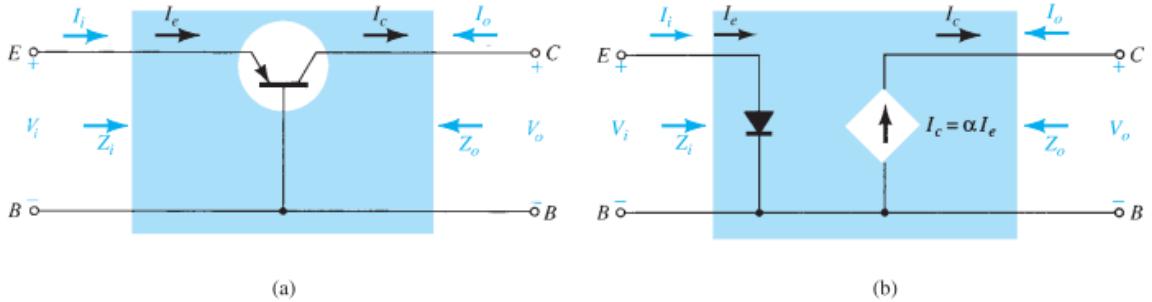
$r_e$  model for the common-emitter transistor configuration including effects of  $r_o$



# The $r_e$ Transistor Model (CB)



**FIG. 5.17**  
(a) Common-base BJT transistor; (b) equivalent circuit for configuration of (a).

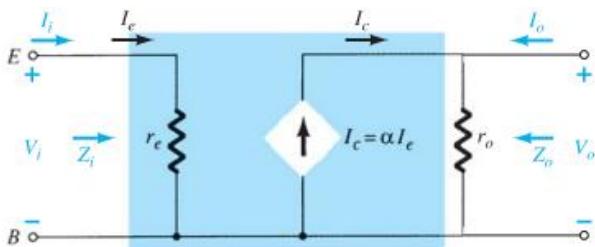

**FIG. 5.18**  
Common base  $r_e$  equivalent circuit.


# The $r_e$ Transistor Model (CC)

- For the common-collector configuration, the model defined for the common-emitter configuration of is normally applied rather than defining a model for the common-collector configuration.


## ***npn versus pnp***

- The dc analysis of *npn* and *pnp* configurations is quite different in the sense that the currents will have opposite directions and the voltages opposite polarities.
- However, for an ac analysis where the signal will progress between positive and negative values, the ac equivalent circuit will be the same.


# C.E. Fixed Bias Configuration

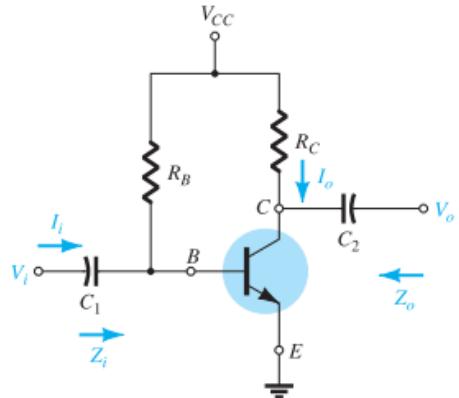
**FIG. 5.20**

Common-emitter fixed-bias configuration.

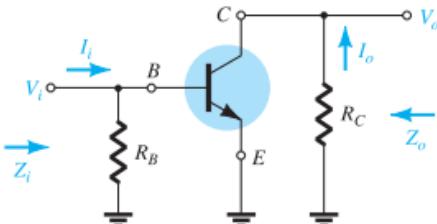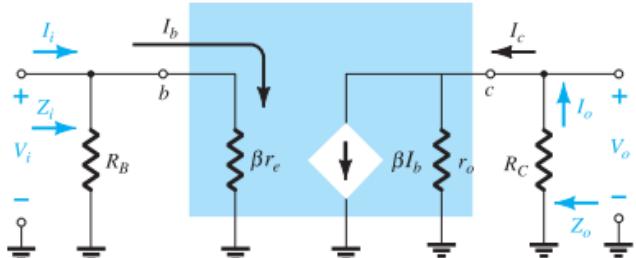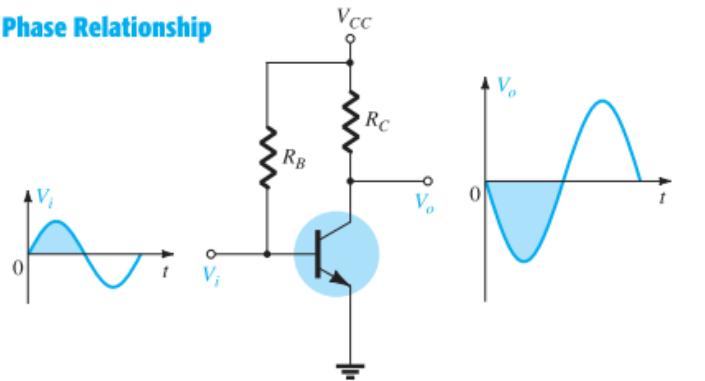

**FIG. 5.21**

Network of Fig. 5.20 following the removal of the effects of  $V_{CC}$ ,  $C_1$ , and  $C_2$ .


**FIG. 5.22**

Substituting the  $r_e$  model into the network of Fig. 5.21.

## Phase Relationship


**FIG. 5.24**


Demonstrating the  $180^\circ$  phase shift between input and output waveforms.

$$Z_i = R_B \parallel \beta r_e \text{ ohms}$$

$$Z_i \approx \beta r_e \quad R_B \geq 10\beta r_o \text{ ohms}$$

$$Z_o = R_C \parallel r_o \text{ ohms}$$

$$Z_o \approx R_C \quad r_o \geq 10R_C$$

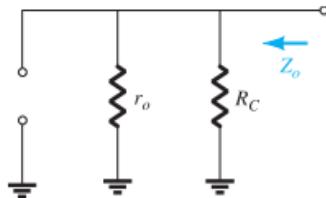
**FIG. 5.23**

Determining  $Z_o$  for the network of Fig. 5.22.

$$V_o = -\beta I_b (R_C \parallel r_o)$$


$$I_b = \frac{V_i}{\beta r_e}$$

$$V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$


$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e}$$

$$A_v = -\frac{R_C}{r_e} \quad r_o \geq 10R_C$$

# Voltage-Divider Bias

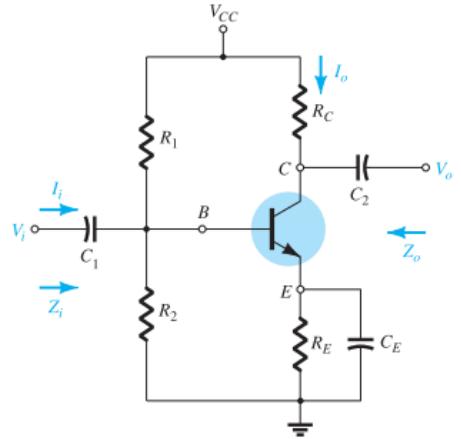**FIG. 5.26**

Voltage-divider bias configuration.

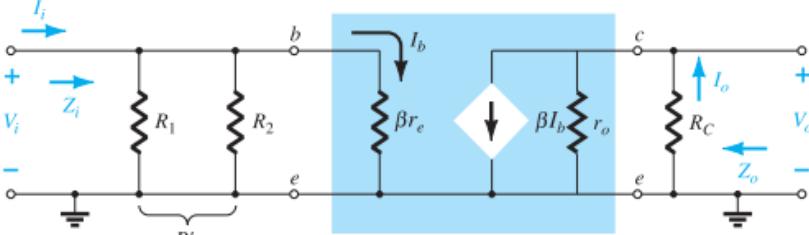**FIG. 5.27**Substituting the  $r_e$  equivalent circuit into the ac equivalent network of Fig. 5.26.

$$R' = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$Z_i = R' \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C \quad r_o \geq 10R_C$$

$$V_o = -(\beta I_b)(R_C \parallel r_o)$$

$$I_b = \frac{V_i}{\beta r_e}$$


$$V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e}$$

180° phase shift

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e} \quad r_o \geq 10R_C$$

# C.E. Emitter Bias Configuration

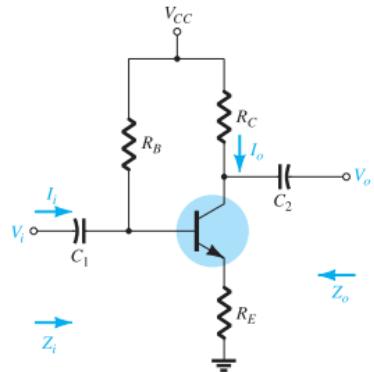**Unbypassed****FIG. 5.29**

CE emitter-bias configuration.

$$V_i = I_b \beta r_e + I_e R_E$$



$$V_i = I_b \beta r_e + (\beta + 1) I_b R_E$$

$$Z_b = \frac{V_i}{I_b} = \beta r_e + (\beta + 1) R_E$$

$$Z_b = \beta r_e + \beta R_E$$

$$Z_b \cong \beta(r_e + R_E)$$

$$Z_b \cong \beta R_E$$

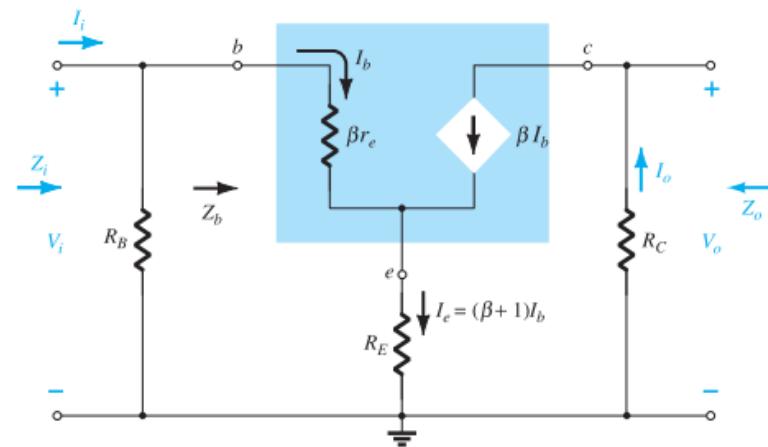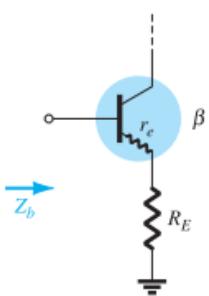**FIG. 5.30**Substituting the  $r_e$  equivalent circuit into the ac equivalent network of Fig. 5.29.**FIG. 5.31**

Defining the input impedance of a transistor with an unbypassed emitter resistor.

$$Z_i = R_B \parallel Z_b$$

$$Z_o = R_C$$

$$I_b = \frac{V_i}{Z_b}$$

$$V_o = -I_o R_C = -\beta I_b R_C \\ = -\beta \left( \frac{V_i}{Z_b} \right) R_C$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta R_C}{Z_b}$$

$$Z_b \cong \beta R_E$$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{R_E}$$

$$Z_b \cong \beta R_E$$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{R_E}$$

180° phase shift



# C.E. Emitter Bias Configuration..

## Effect of $r_o$

$$Z_b = \beta r_e + \left[ \frac{(\beta + 1) + R_C/r_o}{1 + (R_C + R_E)/r_o} \right] R_E$$

$R_C/r_o$  is always much less than  $(\beta + 1)$ ,

$$Z_b \cong \beta r_e + \frac{(\beta + 1)R_E}{1 + (R_C + R_E)/r_o}$$

For  $r_o \geq 10(R_C + R_E)$ ,

$$Z_b \cong \beta(r_e + R_E)$$

$$Z_b \cong \beta(r_e + R_E) \quad r_o \geq 10(R_C + R_E)$$

$$Z_o = R_C \parallel \left[ r_o + \frac{\beta(r_o + r_e)}{1 + \frac{\beta r_e}{R_E}} \right]$$

$$A_v = \frac{V_o}{V_i} = \frac{-\frac{\beta R_C}{Z_b} \left[ 1 + \frac{r_e}{r_o} \right] + \frac{R_C}{r_o}}{1 + \frac{R_C}{r_o}}$$

$$\frac{r_e}{r_o} \ll 1,$$


$$Z_o \cong R_C \parallel r_o \left[ 1 + \frac{\beta}{1 + \frac{\beta r_e}{R_E}} \right]$$

$$Z_o \cong R_C \parallel r_o \left[ 1 + \frac{1}{\frac{1}{\beta} + \frac{r_e}{R_E}} \right]$$

$$A_v = \frac{V_o}{V_i} \cong \frac{-\frac{\beta R_C}{Z_b} + \frac{R_C}{r_o}}{1 + \frac{R_C}{r_o}}$$

$$r_o \geq 10R_C,$$
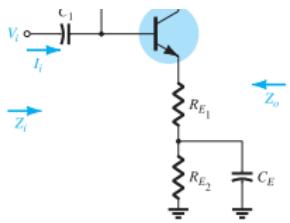
$$A_v = \frac{V_o}{V_i} \cong -\frac{\beta R_C}{Z_b} \quad r_o \geq 10R_C$$



Bypassed


Same as CE fixed bias config.

FIG. 5.35


An emitter-bias configuration with a portion of the emitter-bias resistance bypassed in the ac domain.



# Emitter Follower Configuration

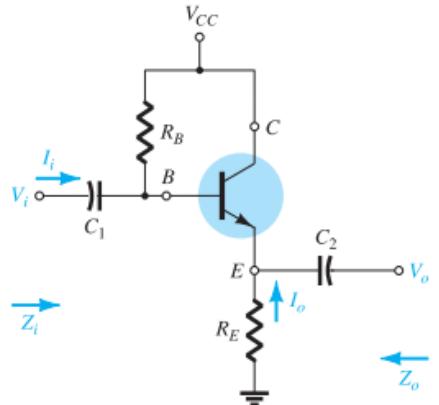

**FIG. 5.36**  
Emitter-follower configuration.

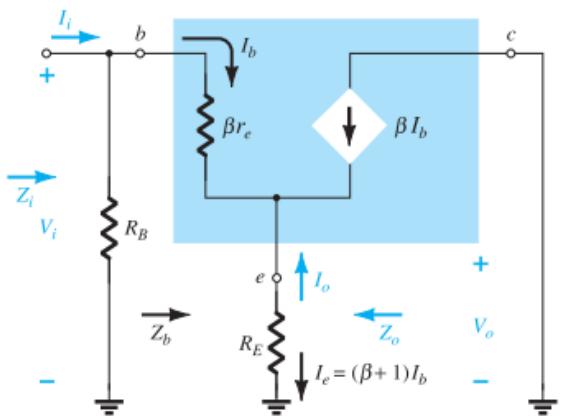

Substituting the  $r_e$  equivalent circuit into the ac equivalent network of Fig. 5.36.

$$Z_i = R_B \parallel Z_b$$

$$Z_b = \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta(r_e + R_E)$$

$$Z_b \cong \beta R_E \quad R_E \gg r_e$$

$$V_o = \frac{R_E V_i}{R_E + r_e}$$

$$A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e}$$

Because  $R_E$  is usually much greater than  $r_e$ ,

$$R_E + r_e \cong R_E :$$

$$I_e = (\beta + 1)I_b = (\beta + 1) \frac{V_i}{Z_b}$$

$$I_e = \frac{(\beta + 1)V_i}{\beta r_e + (\beta + 1)R_E}$$

$$A_v = \frac{V_o}{V_i} \cong 1$$

in phase


$$I_e = \frac{V_i}{[\beta r_e / (\beta + 1)] + R_E}$$

$$(\beta + 1) \cong \beta$$

$$\frac{\beta r_e}{\beta + 1} \cong \frac{\beta r_e}{\beta} = r_e$$

$$I_e \cong \frac{V_i}{r_e + R_E}$$

$$Z_o = R_E \parallel r_e$$

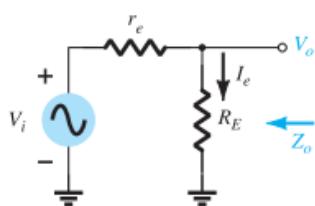

$$Z_o \cong r_e$$

**FIG. 5.38**  
Defining the output impedance for the emitter-follower configuration.

# Emitter Follower Configuration..

## Effect of $r_o$

$$Z_b = \beta r_e + \frac{(\beta + 1)R_E}{1 + \frac{R_E}{r_o}}$$

$$r_o \geq 10R_E$$

$$Z_b = \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta(r_e + R_E) \quad r_o \geq 10R_E$$

$$Z_o = r_o \| R_E \| \frac{\beta r_e}{(\beta + 1)}$$

$$Z_o = r_o \| R_E \| r_e$$

$$A_v = \frac{(\beta + 1)R_E/Z_b}{1 + \frac{R_E}{r_o}}$$

$$A_v \cong \frac{\beta R_E}{Z_b}$$

$$Z_o \cong R_E \| r_e \quad \text{Any } r_o$$

$$Z_b \cong \beta(r_e + R_E)$$

$$A_v \cong \frac{\beta R_E}{\beta(r_e + R_E)}$$

$$A_v \cong \frac{R_E}{r_e + R_E} \quad r_o \geq 10R_E$$

# Common-Base Configuration

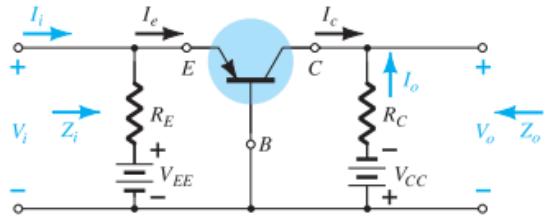


FIG. 5.42

Common-base configuration.

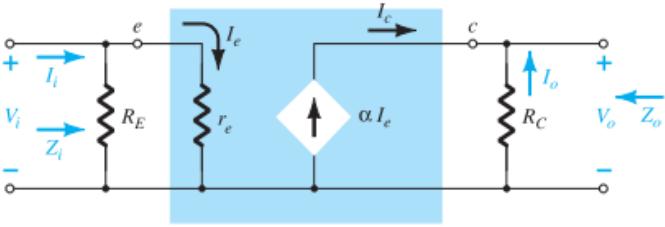


FIG. 5.43

Substituting the  $r_e$  equivalent circuit into the ac equivalent network of Fig. 5.44.

$$Z_i = R_E \parallel r_e$$

$$\begin{aligned} I_e &= I_i \\ I_o &= -\alpha I_e = -\alpha I_i \end{aligned}$$

$$Z_o = R_C$$

$$A_i = \frac{I_o}{I_i} = -\alpha \cong -1$$

$$V_o = -I_o R_C = -(-I_c) R_C = \alpha I_e R_C$$

$$I_e = \frac{V_i}{r_e}$$

$$V_o = \alpha \left( \frac{V_i}{r_e} \right) R_C$$

$$A_v = \frac{V_o}{V_i} = \frac{\alpha R_C}{r_e} \cong \frac{R_C}{r_e}$$

**Phase Relationship** The fact that  $A_v$  is a positive number shows that  $V_o$  and  $V_i$  are in phase for the common-base configuration.

**Effect of  $r_o$**  For the common-base configuration,  $r_o = 1/h_{ob}$  is typically in the megohm range and sufficiently larger than the parallel resistance  $R_C$  to permit the approximation  $r_o \parallel R_C \cong R_C$ .

# Collector-Feedback Configuration

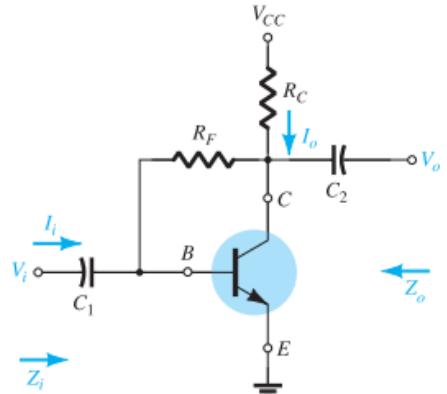


FIG. 5.45

Collector feedback configuration.

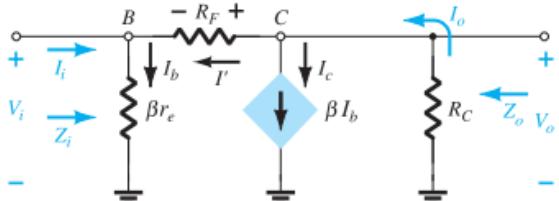


FIG. 5.46

Substituting the  $r_e$  equivalent circuit into the ac equivalent network of Fig. 5.45.

$$I_o = I' + \beta I_b$$

$$I' = I_b - I' = I_b + \beta I_b \frac{(R_C + r_e)}{R_C + R_F}$$

$$I_i = I_b \left( 1 + \beta \frac{(R_C + r_e)}{R_C + R_F} \right)$$

$$Z_i = \frac{V_i}{I_i} = \frac{I_b \beta r_e}{I_b \left( 1 + \beta \frac{(R_C + r_e)}{R_C + R_F} \right)} = \frac{\beta r_e}{1 + \beta \frac{(R_C + r_e)}{R_C + R_F}}$$

$$R_C \gg r_e \quad Z_i = \frac{\beta r_e}{1 + \frac{\beta R_C}{R_C + R_F}}$$

$$I' \left( 1 + \frac{R_C}{R_F} \right) = -\beta I_b \frac{(R_C + r_e)}{R_F}$$

$$I' = -\beta I_b \frac{(R_C + r_e)}{R_C + R_F}$$

$$Z_i = \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_C + R_F}}$$

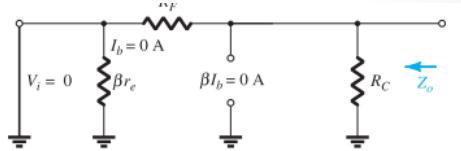


FIG. 5.47

Defining  $Z_o$  for the collector feedback configuration.

$$Z_o \cong R_C \| R_F$$

$$V_o = -I_o R_C = -(I' + \beta I_b) R_C$$

$$= -\left( -\beta I_b \frac{(R_C + r_e)}{R_C + R_F} + \beta I_b \right) R_C$$

$$V_o = -\beta I_b \left( 1 - \frac{(R_C + r_e)}{R_C + R_F} \right) R_C$$

$$A_v = \frac{V_o}{V_i} = \frac{-\beta I_b \left( 1 - \frac{(R_C + r_e)}{R_C + R_F} \right) R_C}{\beta r_e I_b}$$

$$= -\left( 1 - \frac{(R_C + r_e)}{R_C + R_F} \right) \frac{R_C}{r_e}$$

$$A_v = -\left( 1 - \frac{R_C}{R_C + R_F} \right) \frac{R_C}{r_e}$$

$$A_v = -\frac{(R_C + R_F - R_C) R_C}{R_C + R_F - r_e}$$

$$A_v = -\left( \frac{R_F}{R_C + R_F} \right) \frac{R_C}{r_e}$$

$$A_v \cong -\frac{R_C}{r_e}$$

180° phase shift

( 21 )



# Collector-Feedback Configuration..

## Effect of $r_o$

$$Z_i = \frac{1 + \frac{R_C \| r_o}{R_F}}{\frac{1}{\beta r_e} + \frac{1}{R_F} + \frac{R_C \| r_o}{\beta r_e R_F} + \frac{R_C \| r_o}{R_F r_e}}$$

$$r_o \geq 10R_C$$

$$Z_i = \frac{1 + \frac{R_C}{R_F}}{\frac{1}{\beta r_e} + \frac{1}{R_F} + \frac{R_C}{\beta r_e R_F} + \frac{R_C}{R_F r_e}} = \frac{r_e \left[ 1 + \frac{R_C}{R_F} \right]}{\frac{1}{\beta} + \frac{1}{R_F} \left[ r_e + \frac{R_C}{\beta} + R_C \right]}$$

Applying  $R_C \gg r_e$  and  $\frac{R_C}{\beta}$ ,

$$Z_i \cong \frac{r_e \left[ 1 + \frac{R_C}{R_F} \right]}{\frac{1}{\beta} + \frac{R_C}{R_F}} = \frac{r_e \left[ \frac{R_F + R_C}{R_F} \right]}{\frac{R_F + \beta R_C}{\beta R_F}} = \frac{r_e}{\frac{1}{\beta} \left( \frac{R_F}{R_F + R_C} \right) + \frac{R_C}{R_C + R_F}}$$

but, since  $R_F$  typically  $\gg R_C$ ,  $R_F + R_C \cong R_F$  and  $\frac{R_F}{R_F + R_C} = 1$

$$Z_i \cong \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_C + R_F}} \quad r_o \gg R_C, R_F \geq R_C$$

$$Z_o = r_o \| R_C \| R_F$$

For  $r_o \geq 10R_C$ ,

$$Z_o \cong R_C \| R_F \quad r_o \geq 10R_C$$

$$Z_o \cong R_C \quad r_o \geq 10R_C, R_F \gg R_C$$

$$A_v = - \left( \frac{R_F}{R_C \| r_o + R_F} \right) \frac{R_C \| r_o}{r_e}$$

For  $r_o \geq 10R_C$ ,


$$A_v \cong - \left( \frac{R_F}{R_C + R_F} \right) \frac{R_C}{r_e} \quad r_o \geq 10R_C$$

and for  $R_F \gg R_C$

$$A_v \cong - \frac{R_C}{r_e} \quad r_o \geq 10R_C, R_F \geq R_C$$




# Collector DC Feedback Configuration

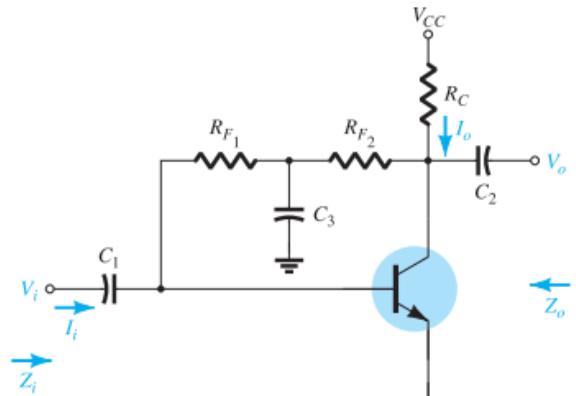

**FIG. 5.50**

Collector dc feedback configuration.

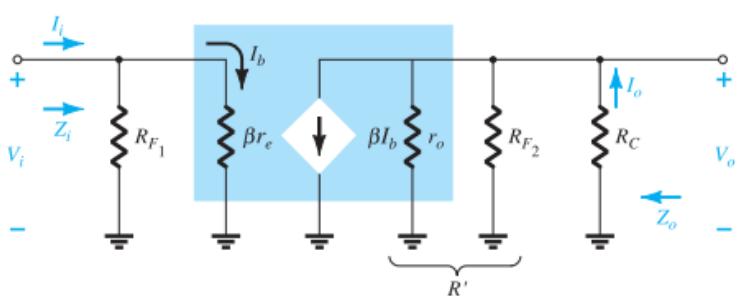

**FIG. 5.51**

Substituting the  $r_e$  equivalent circuit into the ac equivalent network of Fig. 5.50.

$$Z_i = R_{F_1} \parallel \beta r_e$$

$$V_o = -\beta \frac{V_i}{\beta r_e} R'$$

$$Z_o = R_C \parallel R_{F_2} \parallel r_o$$

$$A_v = \frac{V_o}{V_i} = -\frac{r_o \parallel R_{F_2} \parallel R_C}{r_e}$$

$$R' = r_o \parallel R_{F_2} \parallel R_C$$

$$V_o = -\beta I_b R'$$

$$Z_o \cong R_C \parallel R_{F_2} \quad r_o \geq 10R_C$$

$$I_b = \frac{V_i}{\beta r_e}$$

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_{F_2} \parallel R_C}{r_e} \quad r_o \geq 10R_C$$

180° phase shift


( 23 )





# EFFECT OF $R_L$ AND $R_S$ (SYSTEM APPROACH)

# Effect of $R_L$ and $R_s$

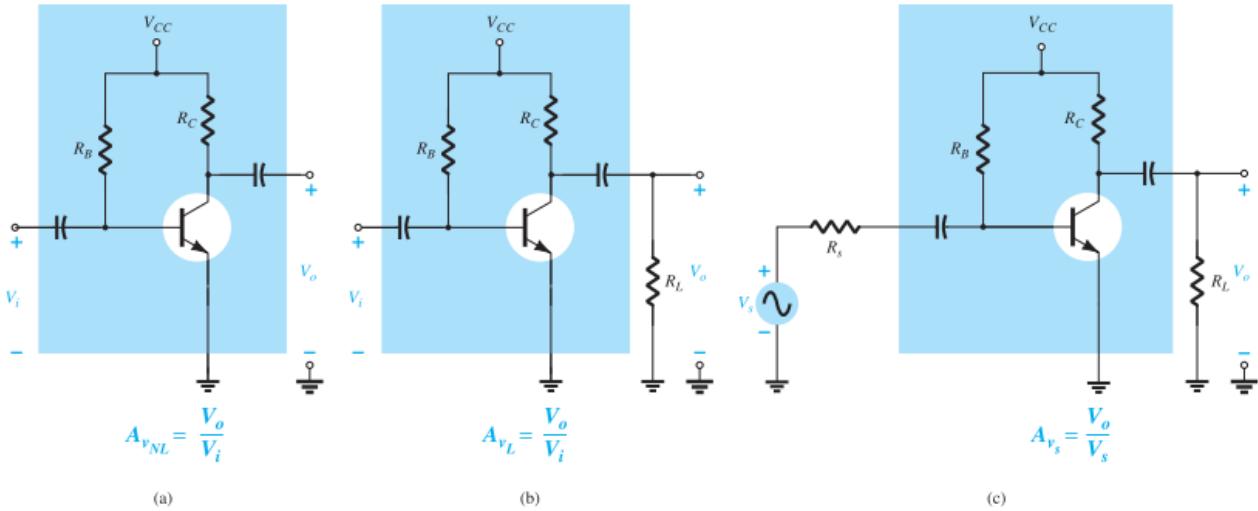**FIG. 5.54**

Amplifier configurations: (a) unloaded; (b) loaded; (c) loaded with a source resistance.

$$A_{v_{NL}} = \frac{V_o}{V_i}$$

$$A_{v_L} = \frac{V_o}{V_i} \quad \text{with } R_L$$

$$A_{v_s} = \frac{V_o}{V_s} \quad \text{with } R_L \text{ and } R_s$$

- The loaded voltage gain of an amplifier is always less than the no-load gain.
- The gain obtained with a source resistance in place will always be less than that obtained under loaded or unloaded conditions due to the drop in applied voltage across the source resistance.
- For the same configuration  $A_{v_{NL}} > A_{v_L} > A_{v_s}$ .
- For a particular design, the larger the level of  $R_L$ , the greater is the level of ac gain.
- For a particular amplifier, the smaller the internal resistance of the signal source, the greater is the overall gain.
- For any network that have coupling capacitors, the source and load resistance do not affect the dc biasing levels.



# Effect of $R_L$ and $R_s$ ..

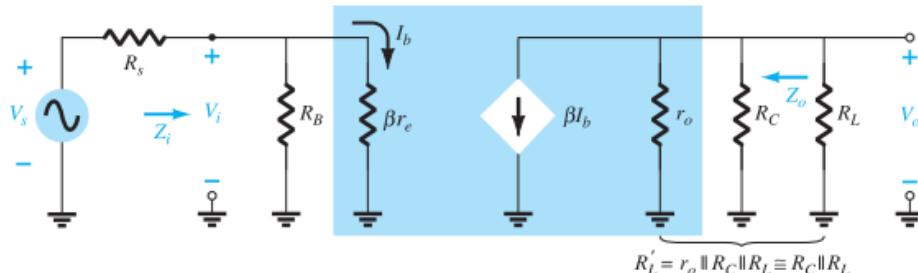


FIG. 5.55

The ac equivalent network for the network of Fig. 5.54c.

$$R'_L = r_o \parallel R_C \parallel R_L \equiv R_C \parallel R_L$$

$$V_o = -\beta I_b R'_L = -\beta I_b (R_C \parallel R_L)$$

$$I_b = \frac{V_i}{\beta r_e}$$

$$V_o = -\beta \left( \frac{V_i}{\beta r_e} \right) (R_C \parallel R_L)$$

$$A_{v_L} = \frac{V_o}{V_i} = -\frac{R_C \parallel R_L}{r_e}$$


$$V_i = \frac{Z_i V_s}{Z_i + R_s}$$

$$\frac{V_i}{V_s} = \frac{Z_i}{Z_i + R_s}$$

$$A_{v_S} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s} = A_{v_L} \frac{Z_i}{Z_i + R_s}$$

$$A_{v_S} = \frac{Z_i}{Z_i + R_s} A_{v_L}$$

## Voltage-divider ct.

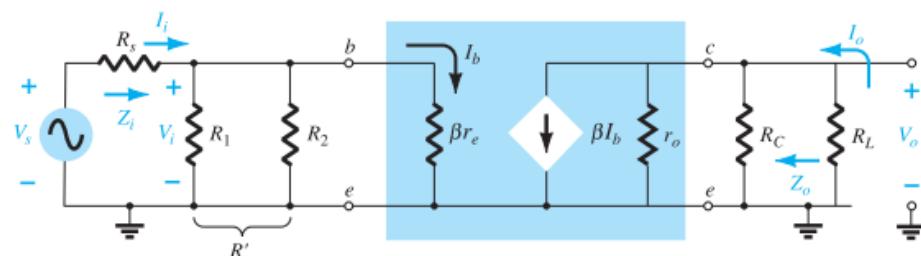

$$Z_i = R_B \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$


$$A_{v_L} = \frac{V_o}{V_i} = -\frac{R_C \parallel R_L}{r_e}$$

$$Z_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

$$A_{v_L} = \frac{V_o}{V_i} = \frac{R_E \parallel R_L}{R_E \parallel R_L + r_e}$$

## Emitter-Follower Ct.

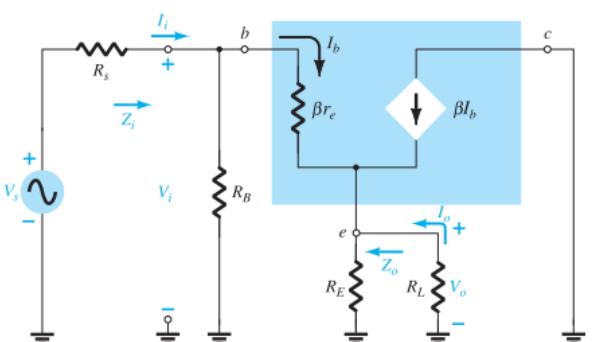

$$Z_i = R_B \parallel Z_b$$

$$Z_b \equiv \beta(R_E \parallel R_L)$$

$$Z_o \equiv r_e$$




( 27 )

# DETERMINING THE CURRENT GAIN



# Determining the Current gain

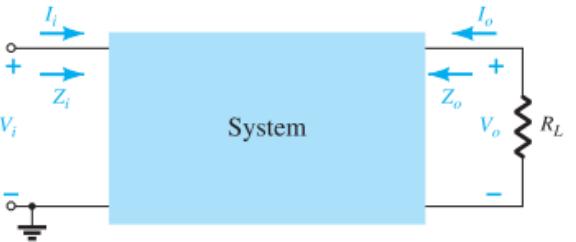**FIG. 5.60**

Determining the current gain using the voltage gain.

- For each transistor configuration, the current gain can be determined directly from the voltage gain, the defined load, and the input impedance.

$$A_i = \frac{I_o}{I_i}$$

$$A_{i_L} = \frac{I_o}{I_i} = \frac{-\frac{V_o}{R_L}}{\frac{V_i}{Z_i}} = -\frac{V_o}{V_i} \cdot \frac{Z_i}{R_L}$$

$$I_i = \frac{V_i}{Z_i} \quad \text{and} \quad I_o = -\frac{V_o}{R_L}$$

$$A_{i_L} = -A_{v_L} \frac{Z_i}{R_L}$$

( 29 )







# SUMMARY TABLE











## Unloaded BJT Transistor Amplifiers

Configuration	$Z_i$	$Z_o$	$A_v$	$A_i$
Fixed-bias:				
	Medium (1 kΩ) $= R_B \parallel \beta r_e$ $\cong \beta r_e$ $(R_B \geq 10\beta r_e)$	Medium (2 kΩ) $= R_C \parallel r_o$ $\cong R_C$ $(r_o \geq 10R_C)$	High (-200) $= -\frac{(R_C \parallel r_o)}{r_e}$ $\cong -\frac{R_C}{r_e}$ $(r_o \geq 10R_C)$	High (100) $= \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)}$ $\cong \beta$ $(r_o \geq 10R_C,$ $R_B \geq 10\beta r_e)$
Voltage-divider bias:				
	Medium (1 kΩ) $= R_1 \parallel R_2 \parallel \beta r_e$	Medium (2 kΩ) $= R_C \parallel r_o$ $\cong R_C$ $(r_o \geq 10R_C)$	High (-200) $= -\frac{R_C \parallel r_o}{r_e}$ $\cong -\frac{R_C}{r_e}$ $(r_o \geq 10R_C)$	High (50) $= \frac{\beta(R_1 \parallel R_2)r_o}{(r_o + R_C)(R_1 \parallel R_2 + \beta r_e)}$ $\cong \frac{\beta(R_1 \parallel R_2)}{R_1 \parallel R_2 + \beta r_e}$ $(r_o \geq 10R_C)$
Unbypassed emitter bias:				
	High (100 kΩ) $= R_B \parallel Z_b$ $Z_b \cong \beta(r_e + R_E)$ $\cong R_B \parallel \beta R_E$ $(R_E \gg r_e)$	Medium (2 kΩ) $= R_C$ $(any level of r_o)$	Low (-5) $= -\frac{R_C}{r_e + R_E}$ $\cong -\frac{R_C}{R_E}$ $(R_E \gg r_e)$	High (50) $\cong -\frac{\beta R_B}{R_B + Z_b}$
Emitter-follower:				
	High (100 kΩ) $= R_B \parallel Z_b$ $Z_b \cong \beta(r_e + R_E)$ $\cong R_B \parallel \beta R_E$ $(R_E \gg r_e)$	Low (20 Ω) $= R_E \parallel r_e$ $\cong r_e$ $(R_E \gg r_e)$	Low ( $\cong 1$ ) $= \frac{R_E}{R_E + r_e}$ $\cong 1$	High (-50) $\cong -\frac{\beta R_B}{R_B + Z_b}$
Common-base:				
	Low (20 Ω) $= R_E \parallel r_e$ $\cong r_e$ $(R_E \gg r_e)$	Medium (2 kΩ) $= R_C$	High (200) $\cong \frac{R_C}{r_e}$	Low (-1) $\cong -1$
Collector feedback:				
	Medium (1 kΩ) $= \frac{r_e}{\frac{1}{\beta} + \frac{R_C}{R_F}}$ $\cong R_C \parallel R_F$ $(r_o \geq 10R_C)$	Medium (2 kΩ) $\cong R_C \parallel R_F$ $(r_o \geq 10R_C)$	High (-200) $\cong -\frac{R_C}{r_e}$ $(r_o \geq 10R_C)$ $(R_F \gg R_C)$	High (50) $= \frac{\beta R_F}{R_F + \beta R_C}$ $\cong \frac{R_F}{R_C}$

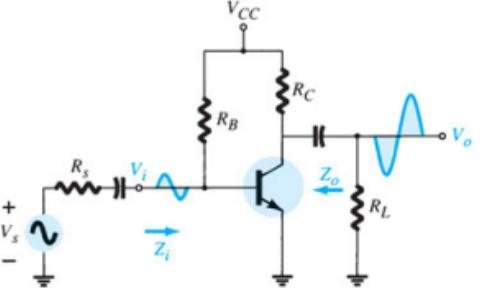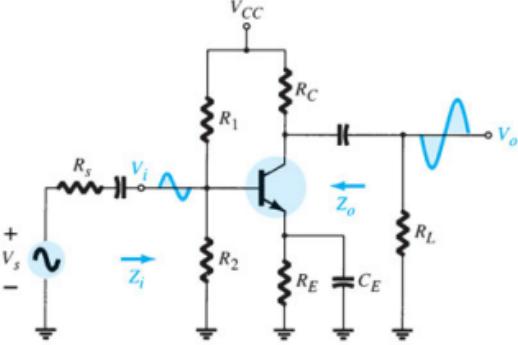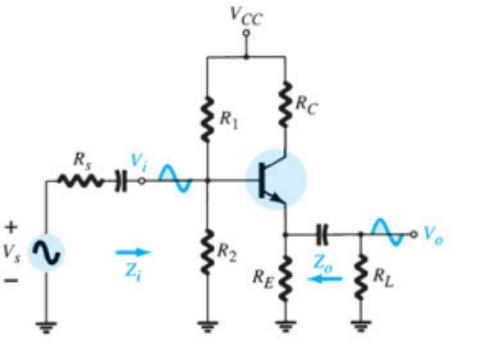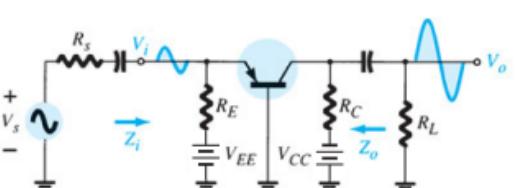Configuration	$A_{v_L} = V_o/V_i$	$Z_i$	$Z_o$
	$\frac{-(R_L \parallel R_C)}{r_e}$	$R_B \parallel \beta r_e$	$R_C$
	Including $r_o$ :	$R_B \parallel \beta r_e$	$R_C \parallel r_o$
	$\frac{-(R_L \parallel R_C)}{r_e}$	$R_1 \parallel R_2 \parallel \beta r_e$	$R_C$
	Including $r_o$ :	$R_1 \parallel R_2 \parallel \beta r_e$	$R_C \parallel r_o$
	$\equiv 1$	$R'_E = R_L \parallel R_E$ $R_1 \parallel R_2 \parallel \beta(r_e + R'_E)$	$R'_s = R_s \parallel R_1 \parallel R_2$ $R_E \parallel \left( \frac{R'_s}{\beta} + r_e \right)$
	Including $r_o$ :	$\equiv 1$	$R_1 \parallel R_2 \parallel \beta(r_e + R'_E)$
	$\equiv \frac{-(R_L \parallel R_C)}{r_e}$	$R_E \parallel r_e$	$R_C$
	Including $r_o$ :	$\equiv \frac{-(R_L \parallel R_C \parallel r_o)}{r_e}$	$R_E \parallel r_e$



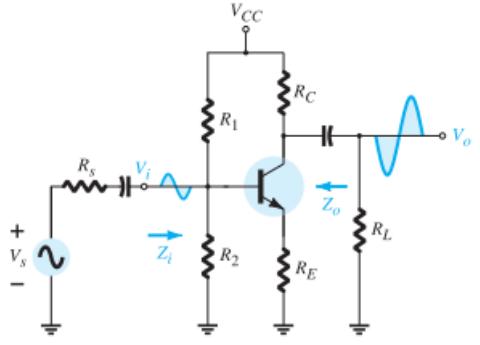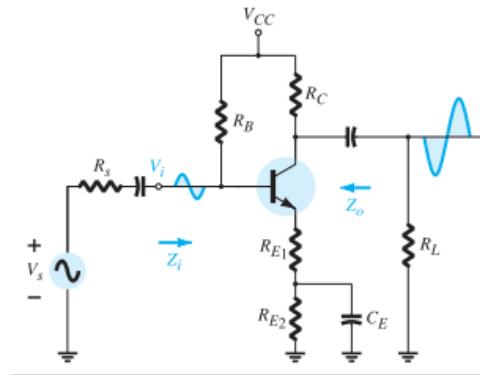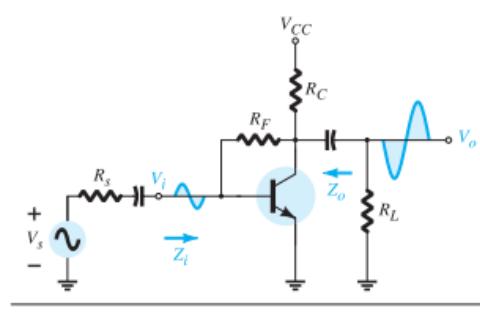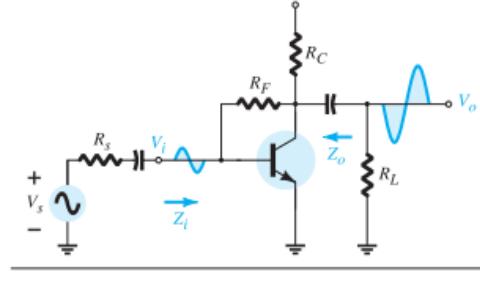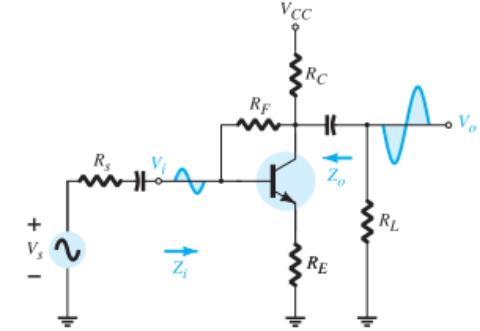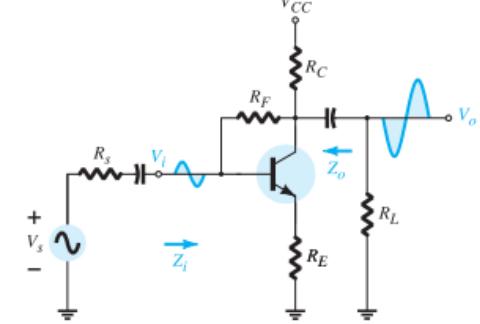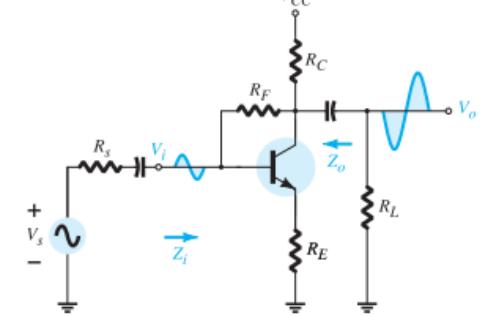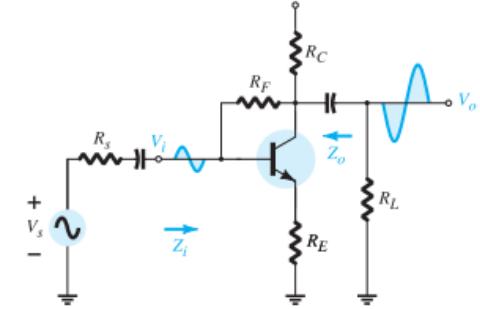

	$\frac{-(R_L \  R_C)}{R_E}$ $R_1 \  R_2 \  \beta(r_e + R_E)$ $R_C$	
Including $r_o$ : 	$\frac{-(R_L \  R_C)}{R_E}$ $R_1 \  R_2 \  \beta(r_e + R_E)$ $\cong R_C$	
	$\frac{-(R_L \  R_C)}{R_{E_1}}$ $R_B \  \beta(r_e + R_{E_1})$ $R_C$	
Including $r_o$ : 	$\frac{-(R_L \  R_C)}{R_{E_t}}$ $R_B \  \beta(r_e + R_E)$ $\cong R_C$	
	$\frac{-(R_L \  R_C)}{r_e}$ $\beta r_e \  \frac{R_F}{ A_v }$ $R_C$	
Including $r_o$ : 	$\frac{-(R_L \  R_C \  r_o)}{r_e}$ $\beta r_e \  \frac{R_F}{ A_v }$ $R_C \  R_F \  r_o$	
	$\frac{-(R_L \  R_C)}{R_E}$ $\beta R_E \  \frac{R_F}{ A_v }$ $\cong R_C \  R_F$	
Including $r_o$ : 	$\cong \frac{-(R_L \  R_C)}{R_E}$ $\cong \beta R_E \  \frac{R_F}{ A_v }$ $\cong R_C \  R_F$	



- For more details, refer to:
  - Chapter 5 at R. Boylestad, **Electronic Devices and Circuit Theory**, 11<sup>th</sup> edition, Prentice Hall.
- The lecture is available online at:
  - <http://bu.edu.eg/staff/ahmad.elbanna-courses/11966>
- For inquiries, send to:
  - [ahmad.elbanna@fes.bu.edu.eg](mailto:ahmad.elbanna@fes.bu.edu.eg)