



INTEGRATED TECHNICAL EDUCATION CLUSTER
AT ALAMEERIA

J-601-1448

Electronic Principles

Lecture #12

Sine wave oscillators

Instructor:

Dr. Ahmad El-Banna



Agenda


- Introduction
- Feedback Oscillators
- Oscillators with RC Feedback Circuits
- Oscillators with LC Feedback Circuits
- Crystal-Controlled Oscillators

INTRODUCTION



Introduction

- An **oscillator** is a circuit that produces a periodic waveform on its output with only the dc supply voltage as an input.
 - The output voltage can be either **sinusoidal** or **non sinusoidal**, depending on the type of oscillator.
 - Two major classifications for oscillators are **feedback** oscillators and **relaxation** oscillators.
- an oscillator converts electrical energy from the dc power supply to periodic waveforms.

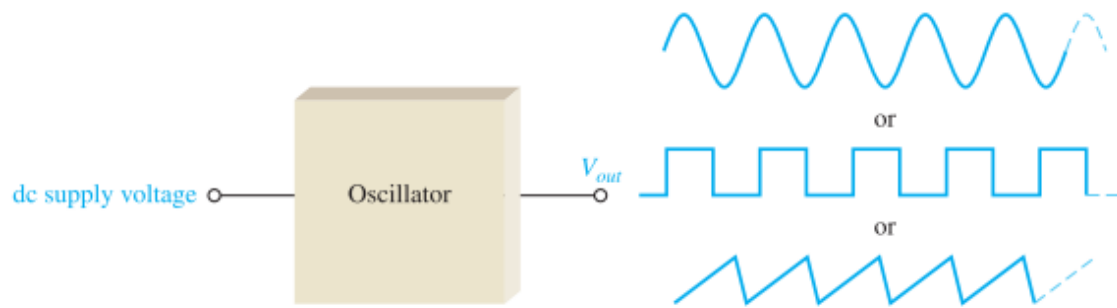


FEEDBACK OSCILLATORS





Positive feedback

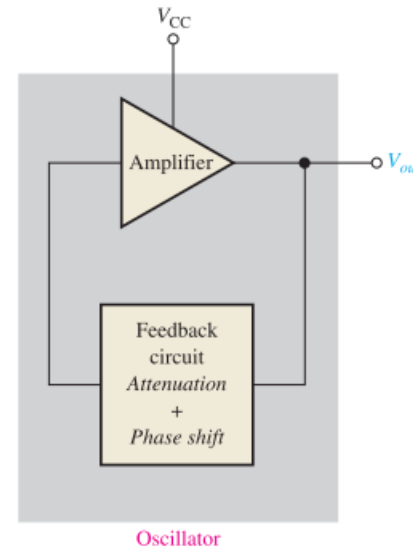- Positive feedback is characterized by the condition wherein a portion of the output voltage of an amplifier is fed back to the input with no net phase shift, resulting in a reinforcement of the output signal.




Basic elements of a feedback oscillator.

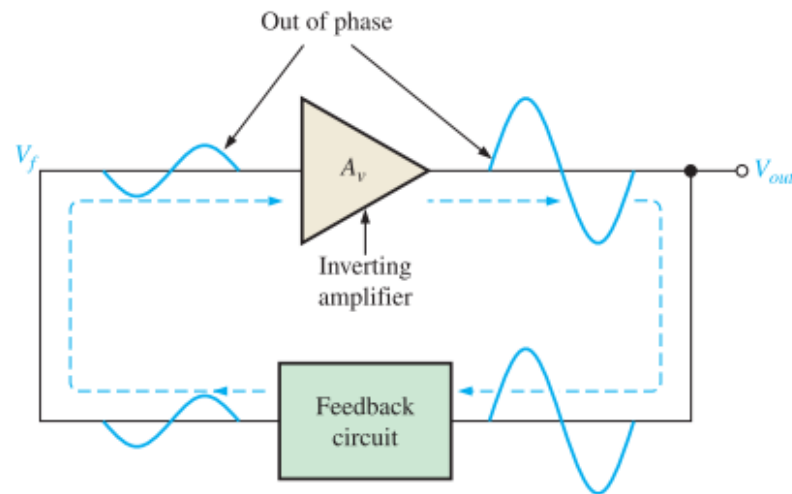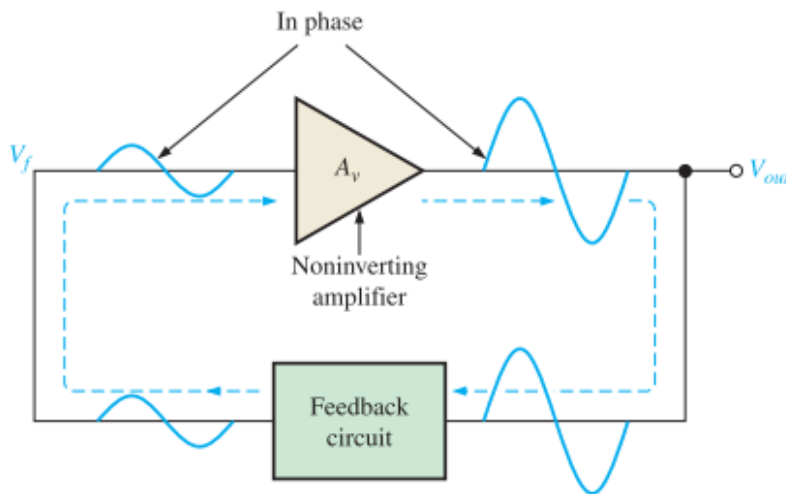


Conditions for Oscillation

- Two conditions:
 1. The phase shift around the feedback loop must be effectively 0° .
 2. The voltage gain, A_{cl} around the closed feedback loop (loop gain) must equal 1 (unity).

$$A_{cl} = A_v B$$

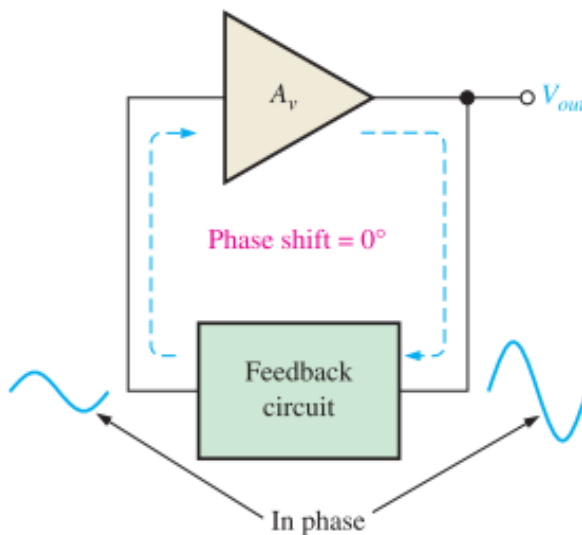

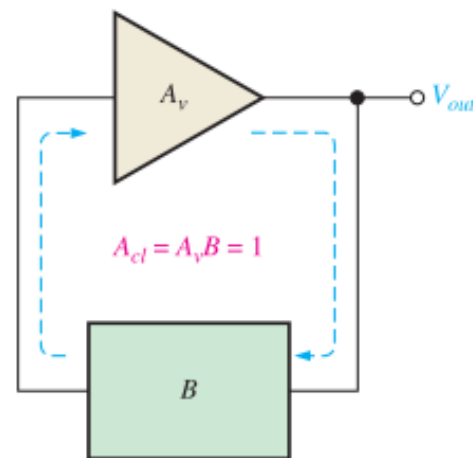
(a) The phase shift around the loop is 0° .



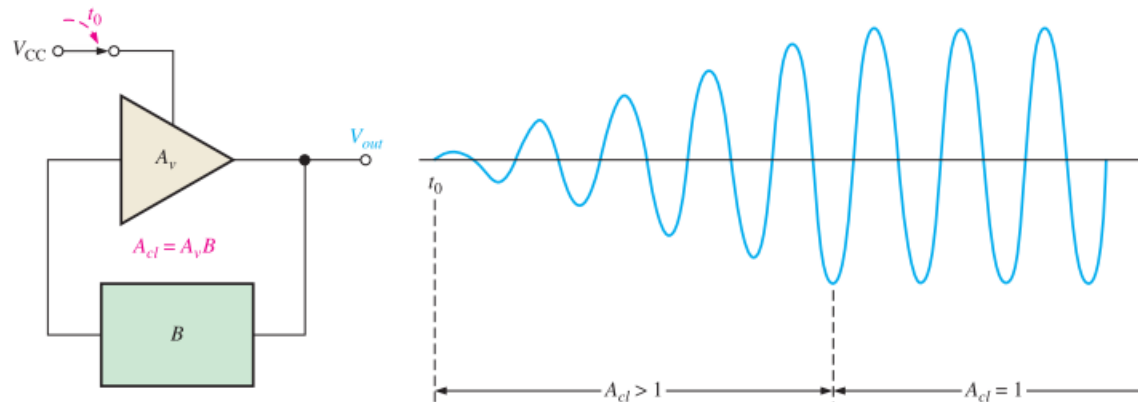(b) The closed loop gain is 1.

Start-Up Conditions

- For oscillation to begin, the voltage gain around the positive feedback loop must be greater than 1 so that the amplitude of the output can build up to a desired level.
- The gain must then decrease to 1 so that the output stays at the desired level and oscillation is sustained.
- Initially, a small positive feedback voltage develops from thermally produced broad-band noise in the resistors or other components or from power supply turn-on transients.



Wien-bridge oscillator

Phase-shift oscillator

Twin-T oscillator

OSCILLATORS WITH RC FEEDBACK CIRCUITS





The Wien-Bridge Oscillator

- Generally, RC feedback oscillators are used for frequencies up to about 1 MHz.
- The Wien-bridge is by far the most widely used type of RC feedback oscillator for this range of frequencies.

$$R_1 = R_2 \text{ and } X_{C1} = X_{C2}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{3}$$


$$f_r = \frac{1}{2\pi RC}$$

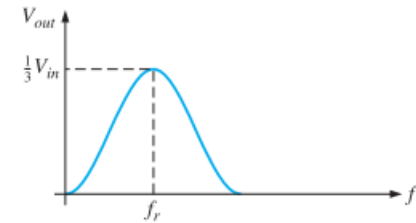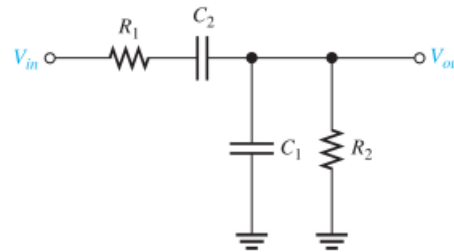


Lead-lag circuit and its response curve

• Basic Circuit
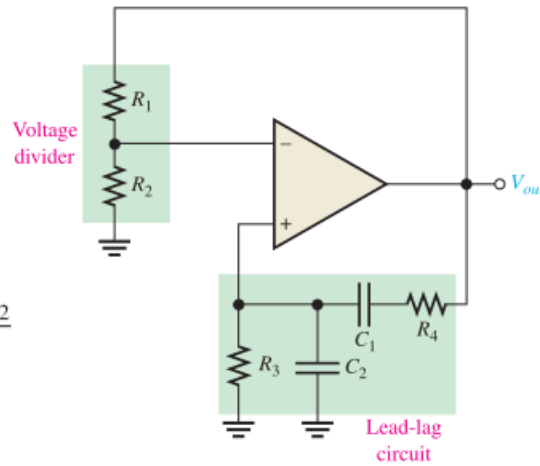
$$A_{cl} = \frac{1}{B} = \frac{1}{R_2/(R_1 + R_2)} = \frac{R_1 + R_2}{R_2}$$



(a)

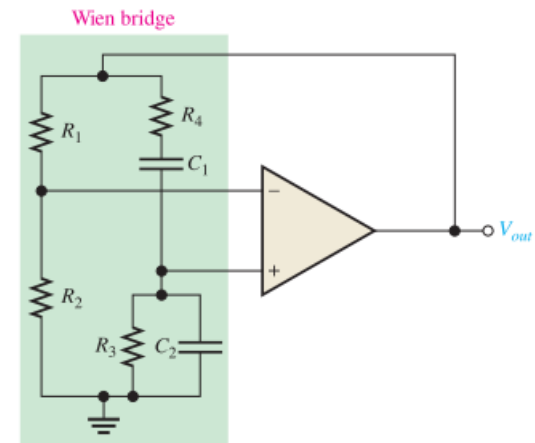

(b) Wien bridge circuit combines a voltage divider and a lead-lag circuit.

▲ FIGURE 16-7

The Wien-bridge oscillator schematic drawn in two different but equivalent ways.


The Wien-Bridge Oscillator..

- Positive Feedback Conditions for Oscillation


$$A_{cl} = 3 \longrightarrow A_{cl} = 1 + (R_1/R_2)$$

choose $R_1 = 2R_2$
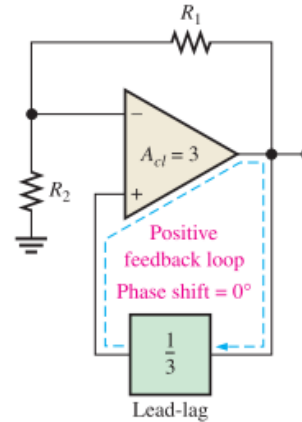
$$A_{cl} = \frac{R_1 + R_2}{R_2} = \frac{2R_2 + R_2}{R_2} = \frac{3R_2}{R_2} = 3$$



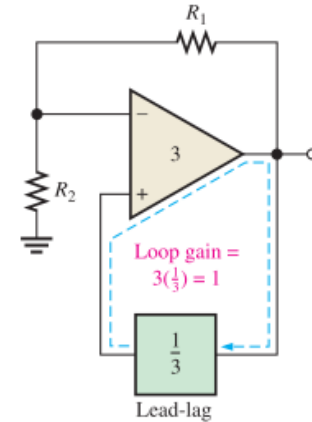
(a) The phase shift around the loop is 0°.




(b) The voltage gain around the loop is 1.

- Start-Up Conditions

$$(A_{cl} > 3)$$

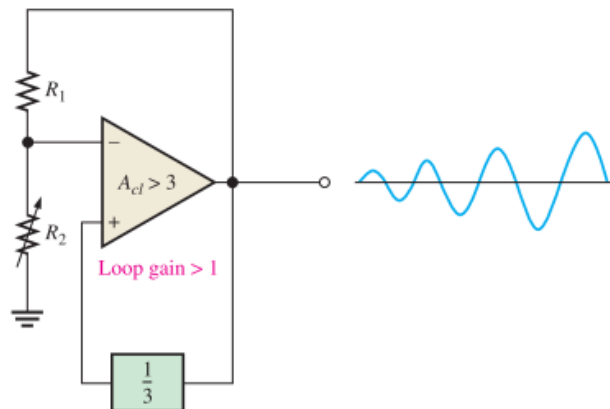

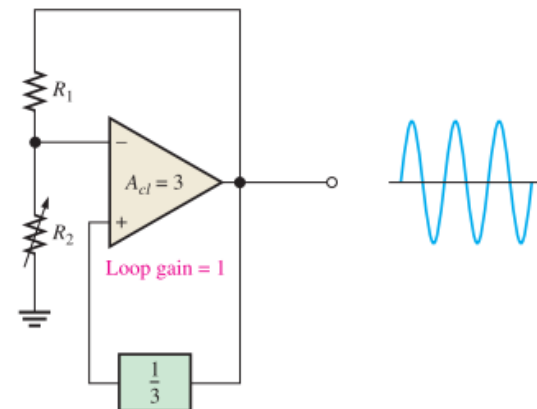(a) Loop gain greater than 1 causes output to build up.



(b) Loop gain of 1 causes a sustained constant output.

Self-starting Wien-bridge oscillator


Using a form of automatic gain control (AGC)

1- When dc power is first applied, both zener diodes appear as opens.

$$A_{cl} = \frac{R_1 + R_2 + R_3}{R_2} = \frac{3R_2 + R_3}{R_2} = 3 + \frac{R_3}{R_2}$$

2- When the zeners conduct, they short out R_3 and $A_{cl} = 3$

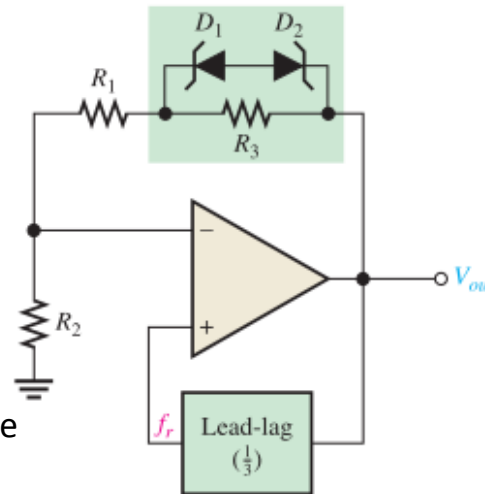- The zener feedback is simple, it suffers from the nonlinearity of the zener diodes that occurs in order to control gain.




◀ FIGURE 16-10

Self-starting Wien-bridge oscillator using back-to-back zener diodes.


▶ FIGURE 16-11

Self-starting Wien-bridge oscillator using a JFET in the negative feedback loop.

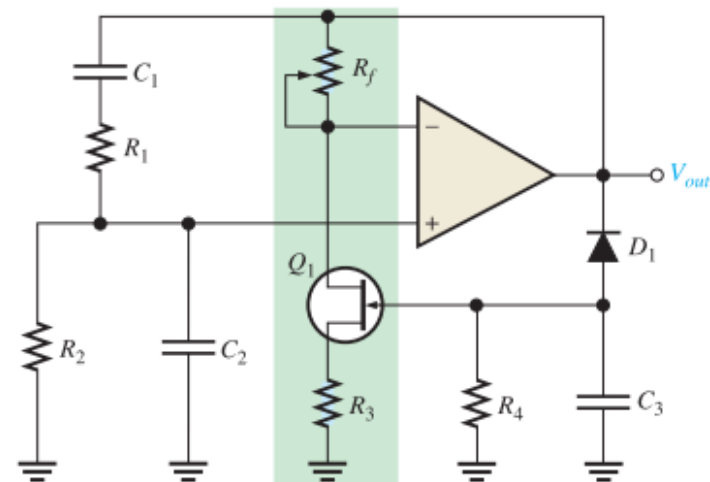
- In some older designs, a tungsten lamp was used in the feed-back circuit to achieve stability.
- A better method to control the gain uses a JFET as a voltage-controlled resistor in a negative feedback path.
- As the voltage increases, the drain-source resistance increases.



The Phase-Shift Oscillator

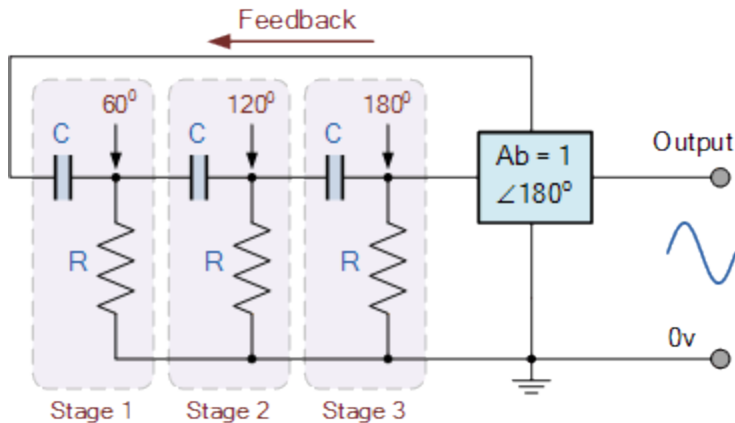

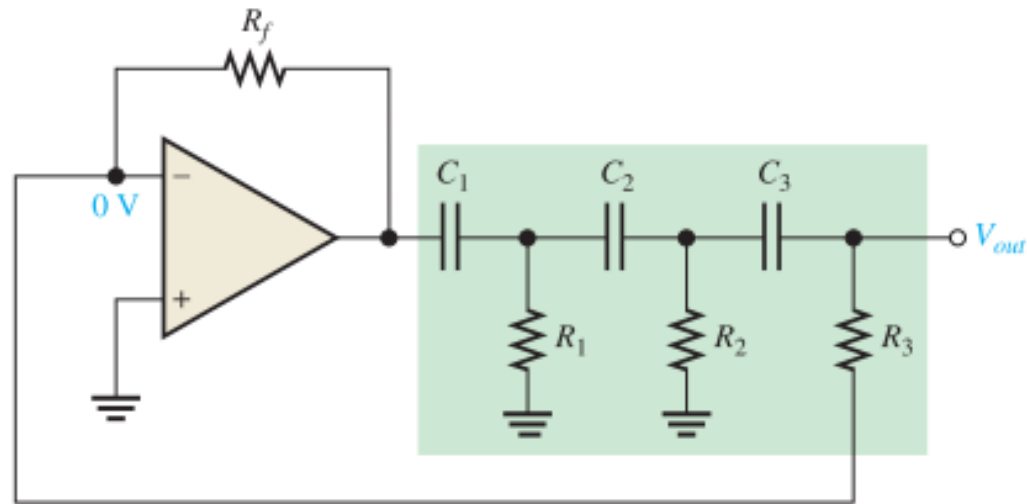- Each of the three RC circuits in the feedback loop can provide a maximum phase shift approaching 90° .
- Oscillation occurs at the frequency where the total phase shift through the three RC circuits is 180° .
- The inversion of the op-amp itself provides the additional 180° to meet the requirement for oscillation of a 360° (or 0°) phase shift around the feedback loop.




$$B = \frac{1}{29} \quad \text{where } B = R_3/R_f.$$

$$R_1 = R_2 = R_3 = R \text{ and } C_1 = C_2 = C_3 = C.$$


$$f_r = \frac{1}{2\pi\sqrt{6RC}}$$

Twin-T Oscillator

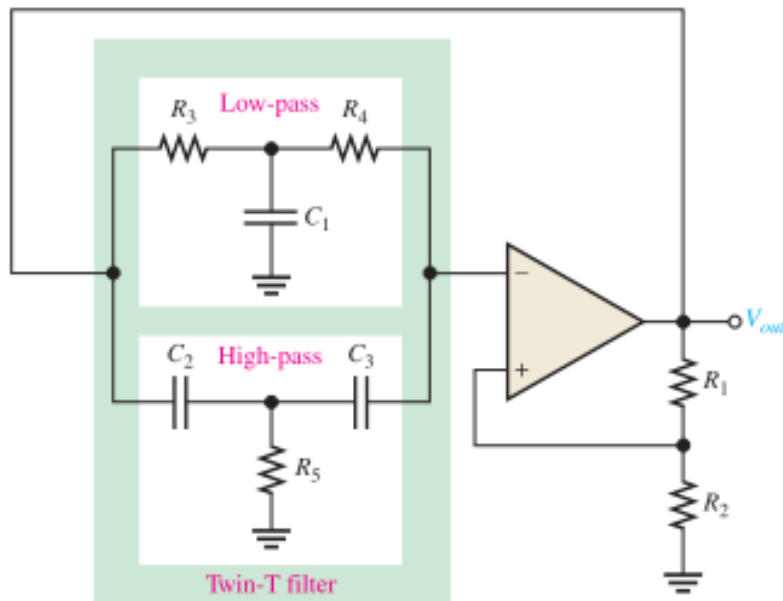- One of the twin-T filters has a low-pass response, and the other has a high-pass response.
- The combined parallel filters produce a band-stop or notch response with a center frequency equal to the desired frequency of oscillation.



(a) Oscillator circuit

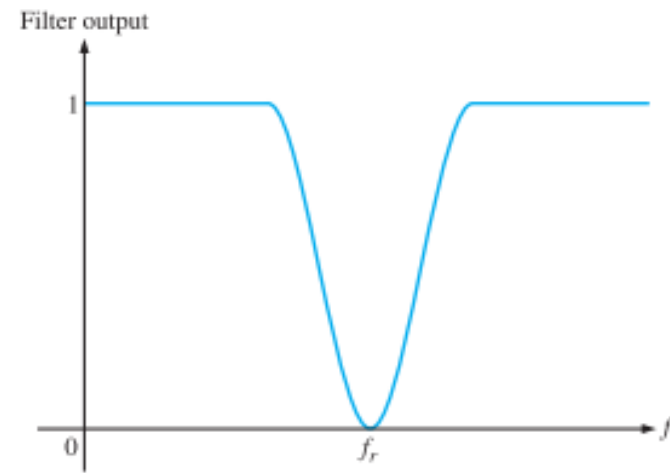

(b) Twin-T filter's frequency response curve

▲ FIGURE 16-15

Twin-T oscillator and twin-T filter response.

THE COLPITTS OSCILLATOR




Colpitts Oscillator

- LC feedback elements are normally used in oscillators that require higher frequencies of oscillation.
- Also, because of the frequency limitation (lower unity-gain frequency) of most op-amps, discrete transistors (BJT or FET) are often used as the gain element in LC oscillators.
- Colpitts oscillator uses an LC circuit in the feedback loop to provide the necessary phase shift and to act as a resonant filter that passes only the desired frequency of oscillation.

$$f_r \cong \frac{1}{2\pi\sqrt{LC_T}}$$

$$C_T = \frac{C_1 C_2}{C_1 + C_2}$$

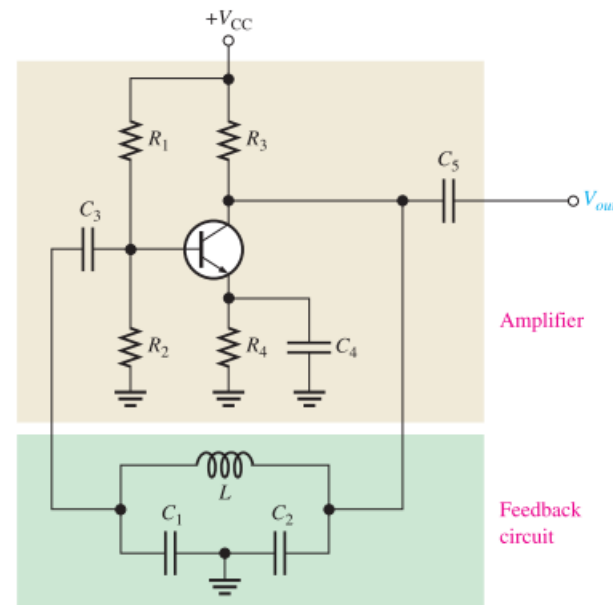

Conditions for Oscillation and Start-Up



$$B = \frac{V_f}{V_{out}} \cong \frac{IX_{C1}}{IX_{C2}} = \frac{X_{C1}}{X_{C2}} = \frac{1/(2\pi f_r C_1)}{1/(2\pi f_r C_2)}$$

$$B = \frac{C_2}{C_1} \quad A_v = \frac{C_1}{C_2}$$

- Loading of the Feedback Circuit Affects the Frequency of Oscillation

→ Z_{in} of the amplifier loads the feed-back circuit and lowers its Q, thus lowering the resonant frequency.

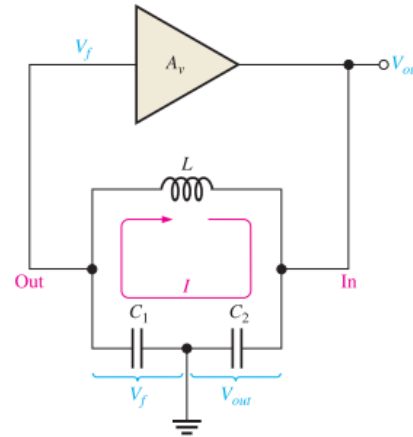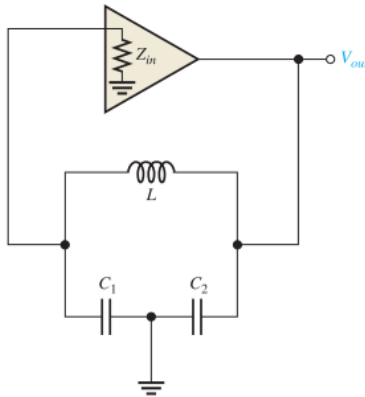
$$f_r = \frac{1}{2\pi\sqrt{LC_T}} \sqrt{\frac{Q^2}{Q^2 + 1}}$$



◀ FIGURE 16-17

The attenuation of the tank circuit is the output of the tank (V_f) divided by the input to the tank (V_{out}). $B = V_f/V_{out} = C_2/C_1$. For $A_v B > 1$, A_v must be greater than C_1/C_2 .

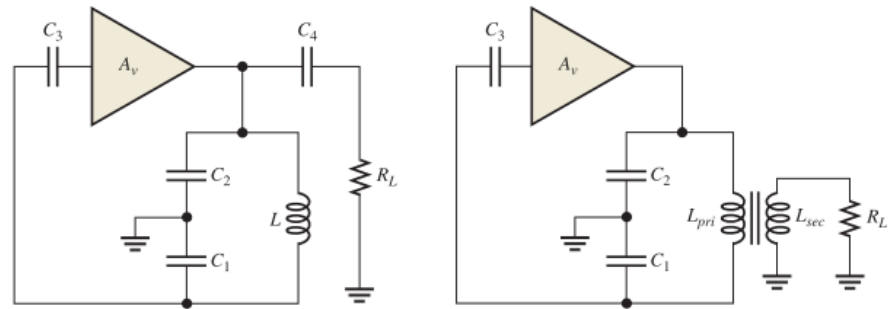→ A FET can be used in place of a BJT, as shown in Figure 16-19, to minimize the loading effect of the transistor's input impedance.



(a) A load capacitively coupled to oscillator output can reduce circuit Q and f_r .
 (b) Transformer coupling of load can reduce loading effect by impedance transformation.

▲ FIGURE 16-20

Oscillator loading.



THE CLAPP OSCILLATOR



Clapp Oscillator


- The Clapp oscillator is a variation of the Colpitts with addition of C_3 .

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

$$(Q > 10) \longrightarrow f_r \cong \frac{1}{2\pi\sqrt{LC_T}}$$

If C_3 is much smaller than C_1 and C_2 ,

$$(f_r \cong 1/(2\pi\sqrt{LC_3})).$$

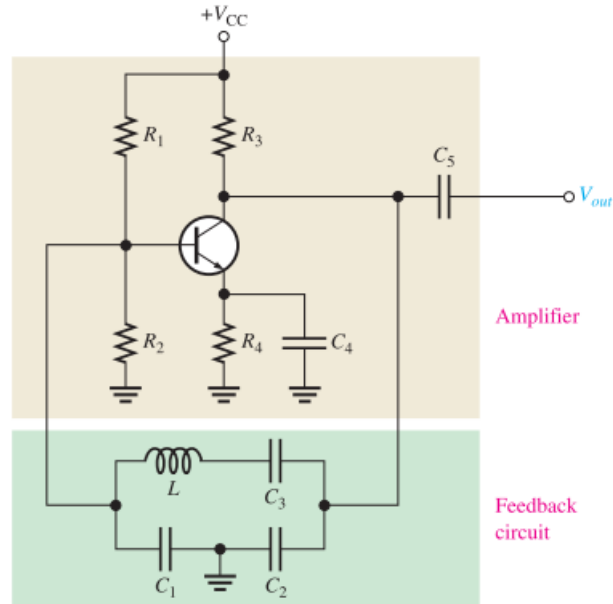

- Since C_1 and C_2 are both connected to ground at one end, the junction capacitance of the transistor and other stray capacitances appear in parallel with C_1 and C_2 to ground, altering their effective values.
- C_3 is not affected, however, and thus provides a more accurate and stable frequency of oscillation.

THE HARTLEY OSCILLATOR



Hartley Oscillator


- The Hartley oscillator is similar to the Colpitts except that the feedback circuit consists of two series inductors and a parallel capacitor

$$Q > 10 \quad f_r \cong \frac{1}{2\pi\sqrt{L_T C}}$$

$$L_T = L_1 + L_2.$$

$$B \cong \frac{L_1}{L_2}$$

$$A_v \cong \frac{L_2}{L_1}$$

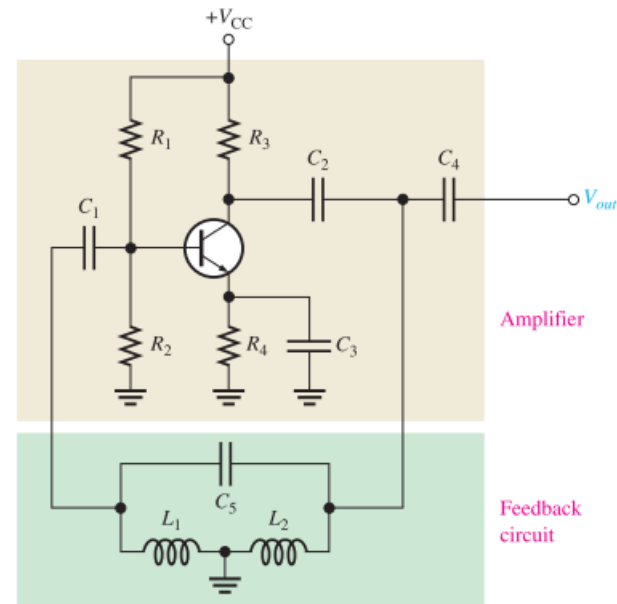

- Loading of the tank circuit has the same effect in the Hartley as in the Colpitts; that is, the Q is decreased and thus f_r decreases.


THE ARMSTRONG OSCILLATOR



Armstrong Oscillator

- This type of LC feedback oscillator uses transformer coupling to feed back a portion of the signal voltage.
- It is sometimes called a “tickler” oscillator in reference to the transformer secondary or “tickler coil” that provides the feedback to keep the oscillation going.
- The Armstrong is less common than the Colpitts, Clapp, and Hartley, mainly because of the disadvantage of transformer size and cost.
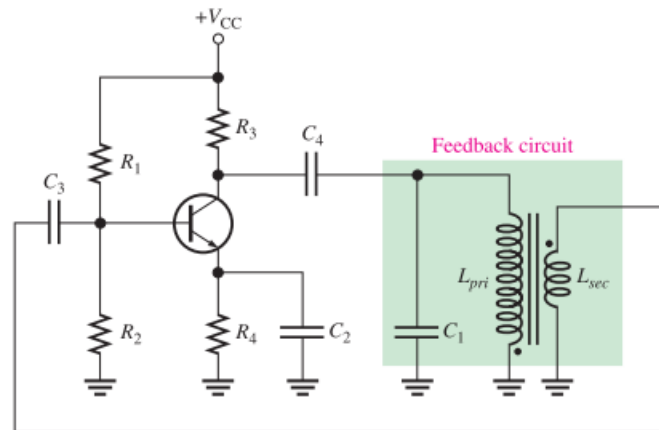
$$f_r = \frac{1}{2\pi\sqrt{L_{pri}C_1}}$$




CRYSTAL-CONTROLLED OSCILLATORS



Crystal-Controlled Oscillators

- The most stable and accurate type of feedback oscillator uses a **piezoelectric crystal** in the feedback loop to control the frequency.
- Quartz is one type of crystalline substance found in nature that exhibits a property called the piezoelectric effect.
- When a changing mechanical stress is applied across the crystal to cause it to vibrate, a voltage develops at the frequency of mechanical vibration.
- Conversely, when an ac voltage is applied across the crystal, it vibrates at the frequency of the applied voltage.
- The greatest vibration occurs at the crystal's natural resonant frequency, which is determined by the physical dimensions and by the way the crystal is cut.


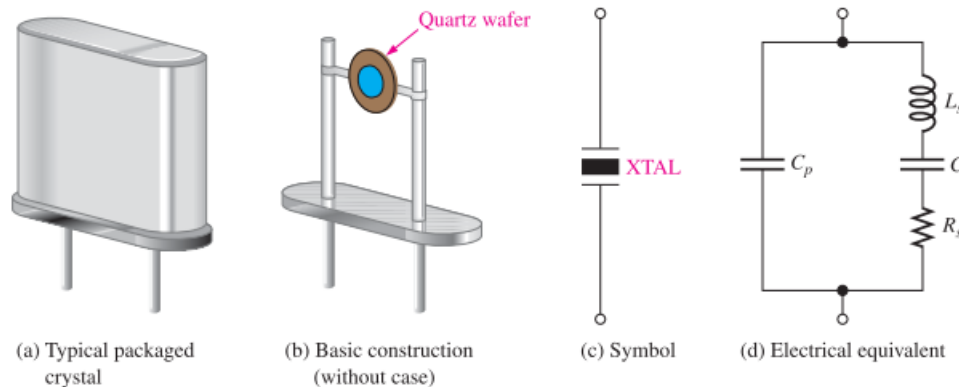


Basic crystal oscillators

- A great advantage of the crystal is that it exhibits a very high Q.
- The impedance of the crystal is minimum at the series resonant frequency, thus providing maximum feedback.
- a crystal is used as a series resonant tank circuit.
- The crystal tuning capacitor, C_c is used to “fine tune” the oscillator frequency by “pulling” the resonant frequency of the crystal slightly up or down.

Modes:

- Piezoelectric crystals can oscillate in either of two modes—fundamental or overtone.
- The **fundamental** frequency of a crystal is the lowest frequency at which it is naturally resonant.
- The fundamental frequency depends on the crystal’s mechanical dimensions, type of cut, .. etc.
- Usually it’s less than 20 MHz.
- **Overtones** are approximate integer multiples of the fundamental frequency.
- Many crystal oscillators are available in integrated circuit packages.

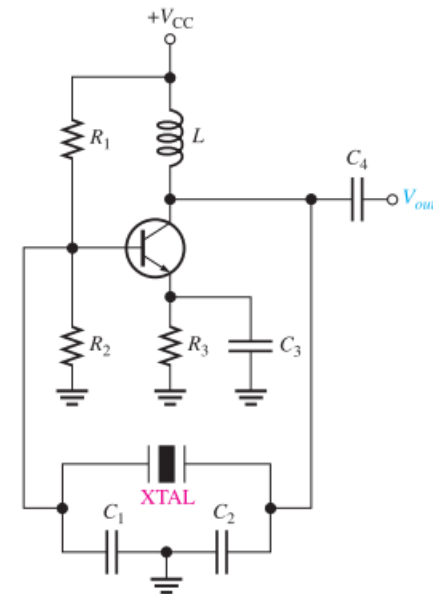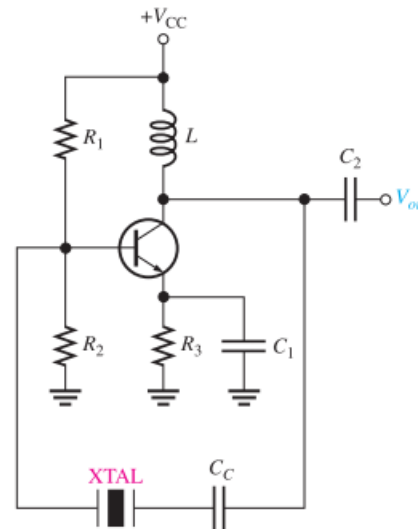

Fall 2014 Course Feedback

Select your course *

- Mobile Communication Systems
- Electronic Circuits (A)
- Electronic Principals
- Engineering Legislations
- Active Circuits
- CAD of Electronics

Feedback link:

<http://goo.gl/forms/ghjNGxQpaj>

The course lies in your area of interest *

- Yes
- No

The course contents had been successfully covered *

- totally agree
- agree
- disagree
- totally disagree

Your evaluation for the instructor *

- excellent
- good
- not bad

- For more details, refer to:
 - Chapter 16 at T. Floyd, **Electronic Devices**, 9th edition.
 - http://www.electronics-tutorials.ws/oscillator/rc_oscillator.html
 - <http://www.electronics-tutorials.ws/oscillator/oscillators.html>
- The lecture is available online at:
 - https://speakerdeck.com/ahmad_elbanna
- For inquiries, send to:
 - ahmad.elbanna@feng.bu.edu.eg