



FACULTY OF ENGINEERING  
DEPARTMENT OF ELECTRONICS AND COMMUNICATIONS

**GEE336**

**Electronic Circuits II**

Lecture #5

Sawtooth & Staircase Generators

**Instructor:**

**Dr. Ahmad El-Banna**



# Grading Strategy

Criteria	Marks	Detailed Marks	Description
Attendance	10	5	Attendance
		5	Participation
Mid Term	40	5	Quiz
		5	Assignment
		30	Written Exam
Final	50	10	Assignment
		40	Written Exam

# Agenda

- Non-Inverting Integrator
- Staircase Generator
- Sawtooth Generator

# NON-INVERTING INTEGRATOR

# Non Inverting Integrator

$$V^+ = V^-$$

- KCL @  $V^-$ :


$$(V_o - V^-)/R = V^- / R$$

So,  $V^- = V_o / 2$

- KCL @  $V^+$ :

$$(V_x - V^+)/R_3 + (V_o - V^+)/R_3 = SC * V^+$$

So,  $V^+ = (V_x + V_o) / (2 + SCR_3)$

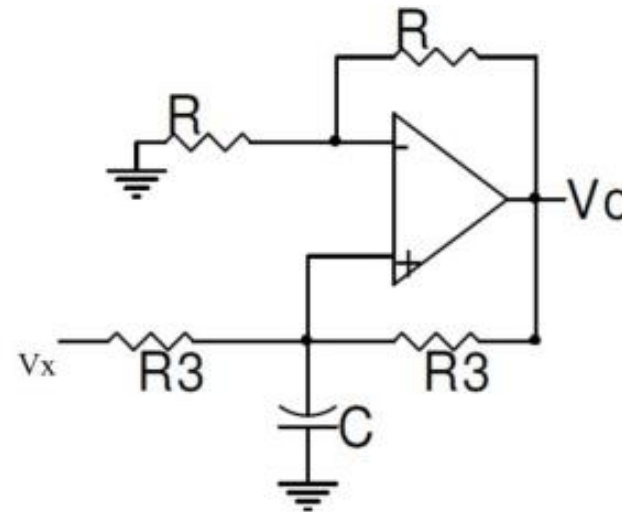

By equating  $V^+$  &  $V^-$  we'll get:

$$V_o = (2/SCR_3) V_x \quad \Rightarrow \text{non-inverting integrator.}$$

Or

$$v_o(t) = (2/CR_3) * \int_0^t v_x dt$$

# Saturation time

## Non Inverting Integrator

assume  $V = 2V$

$$V_o = \frac{2}{5CR} V$$

$$V_o = \frac{2}{CR} \int V dt$$

$$= \frac{2}{CR} \int 2 dt$$

$$= \frac{4}{CR} t = \frac{4}{10^3 \times 10^{-6}} t = 4000 t$$

Saturation time at  $V_o = 5V$

$$5 = 4000 t_{sat}$$



$$t_{sat} = \frac{5}{4000} = 1.25 \text{ ms}$$

at  $t = 1 \text{ ms}$

$$V_o = 4000 \times 10^{-3} = 4V$$

# Saturation time

## Inverting Integrator

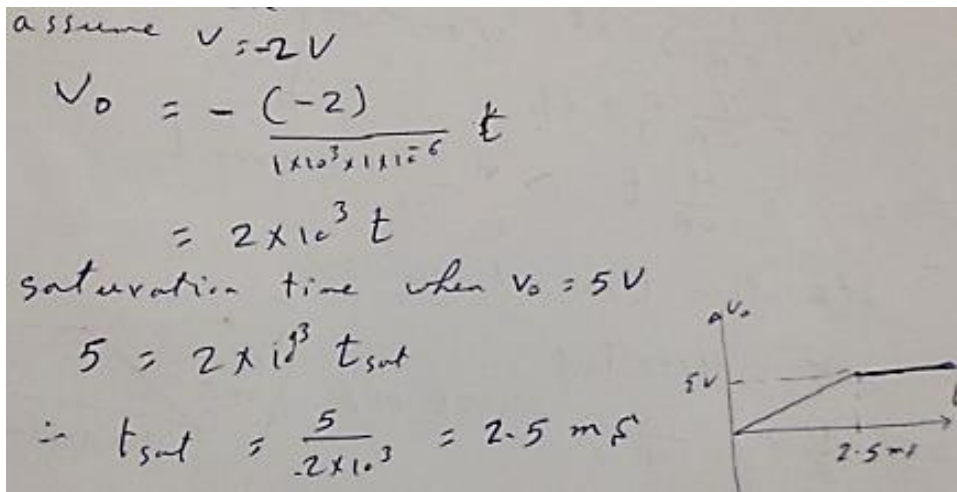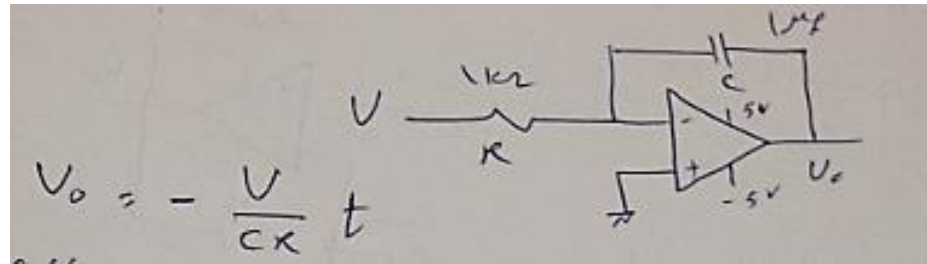


What about  $v = 2v$  ?

# STAIRCASE AND RAMP GENERATOR







# Using BCD Counter

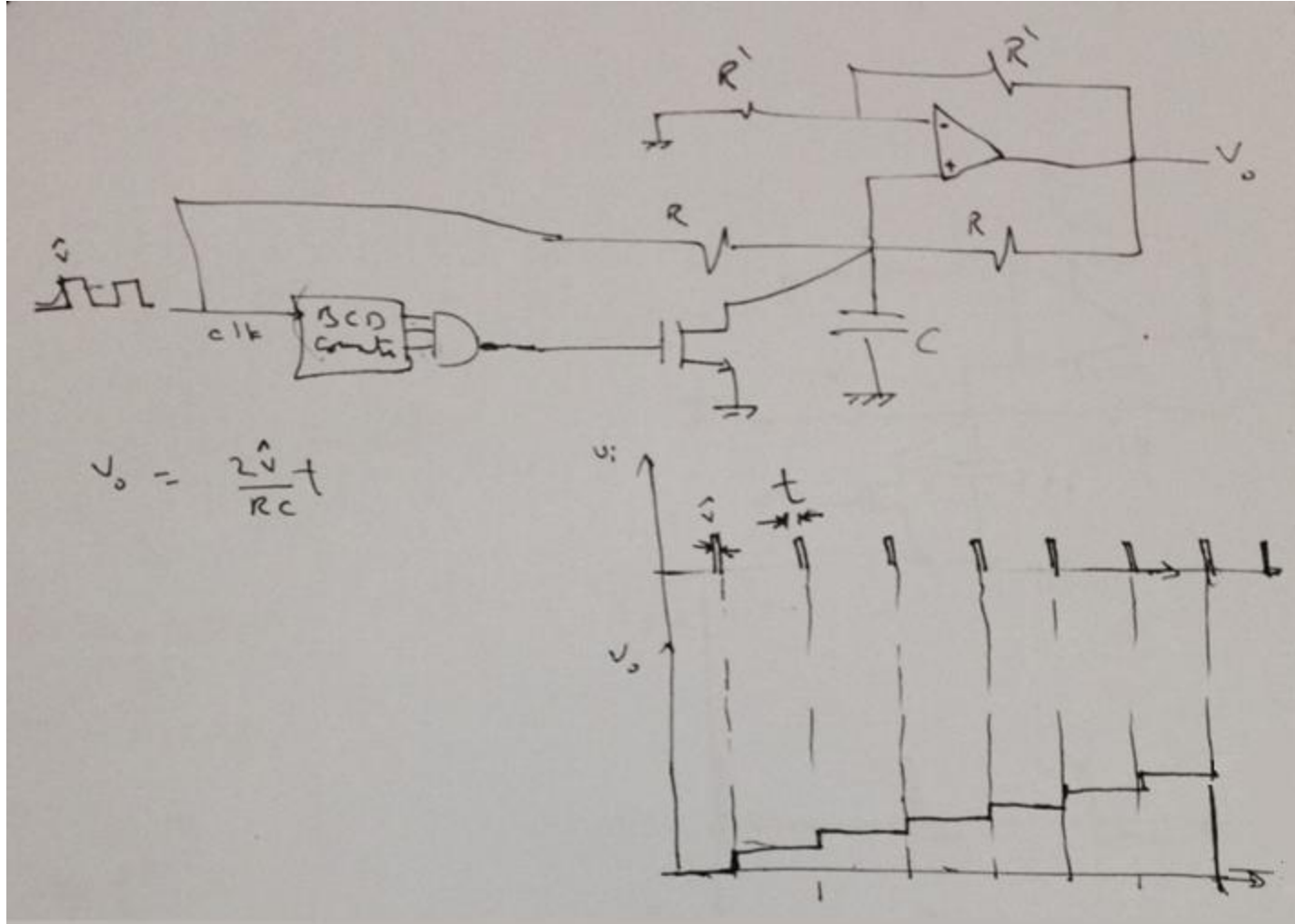


# Staircase Example

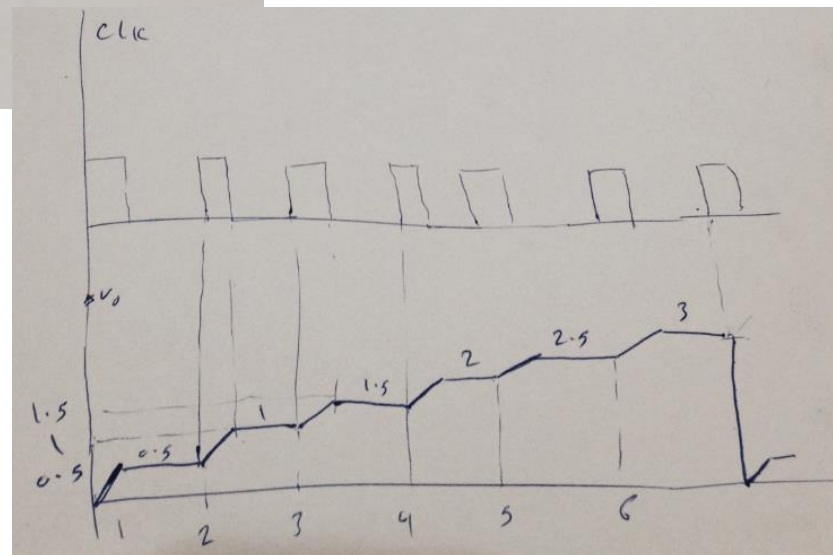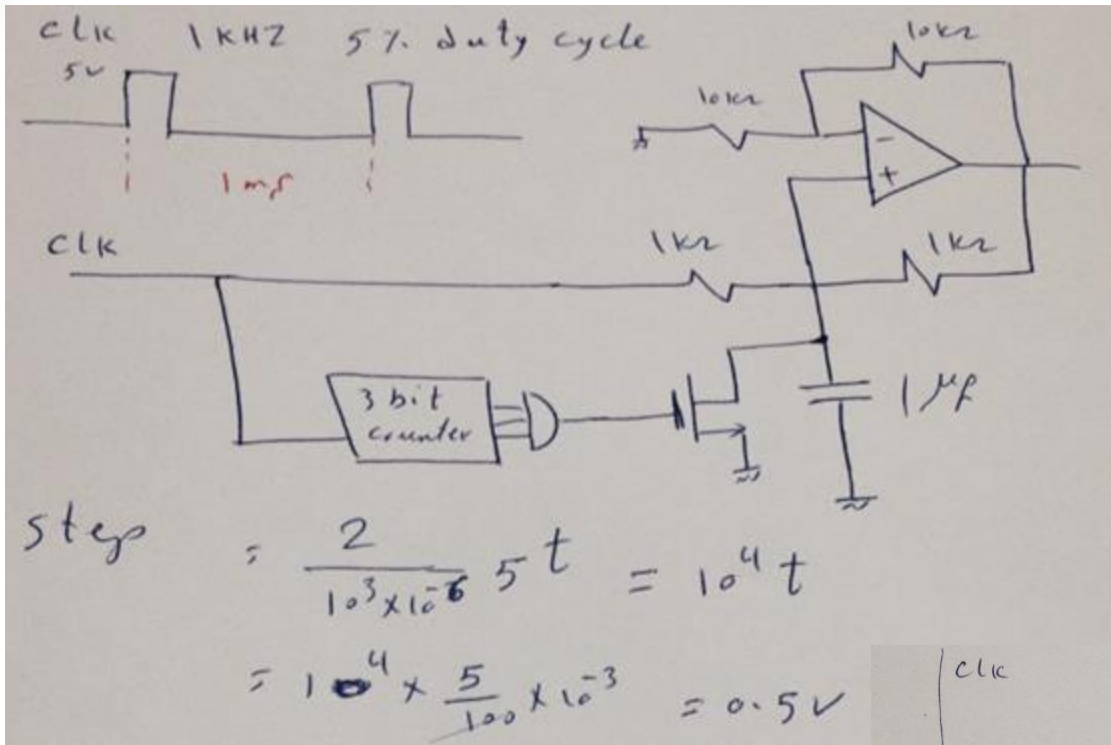


# SAWTOOTH GENERATOR CIRCUITS

# Triangular vs. Sawtooth

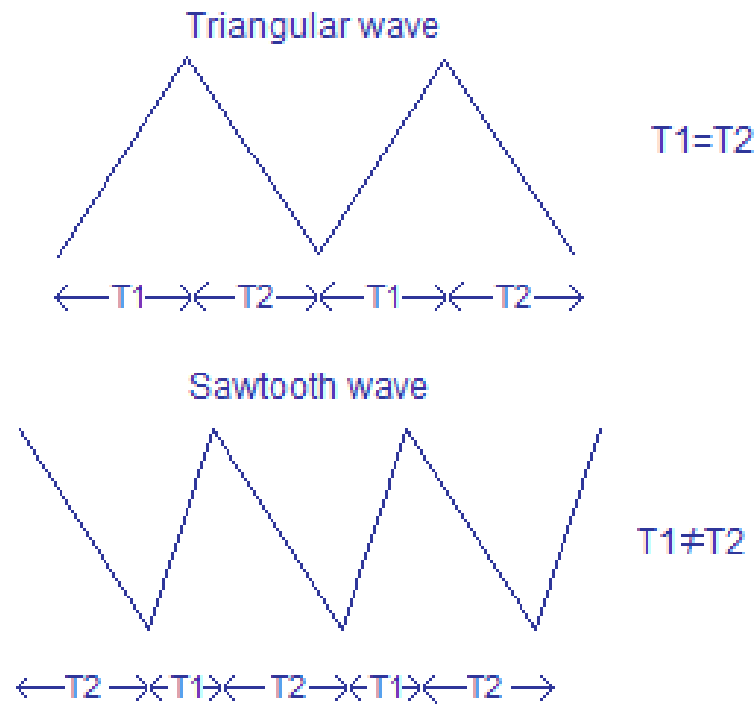

# Sawtooth circuit


Using non inverting Integrator

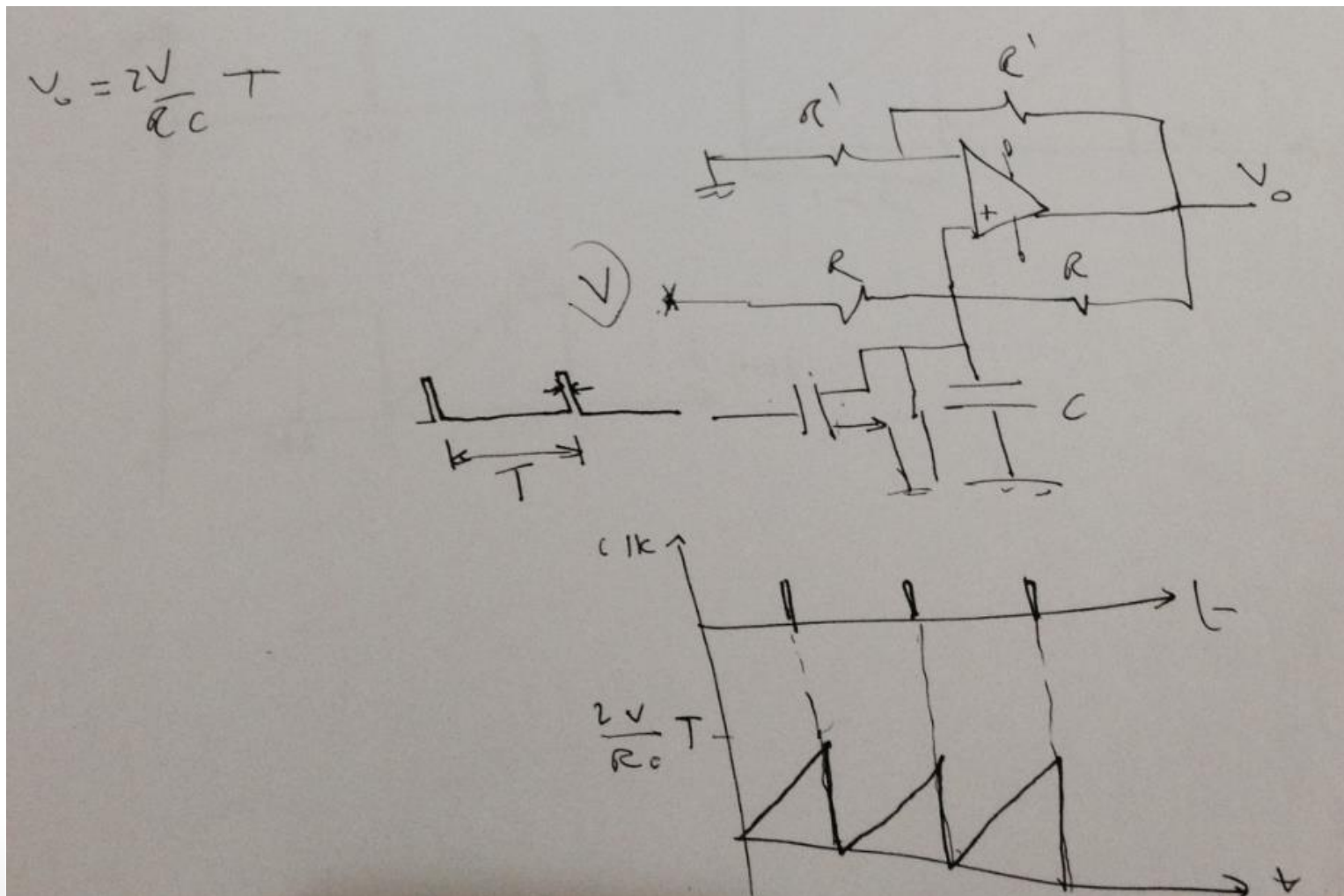


# Sawtooth circuit..

## Astable Multivibrator & Integrator

Stage #1

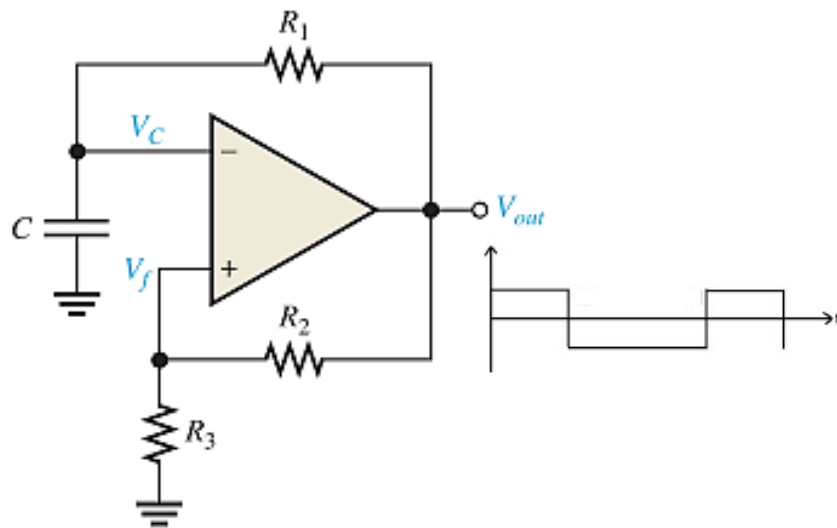


Stage #2

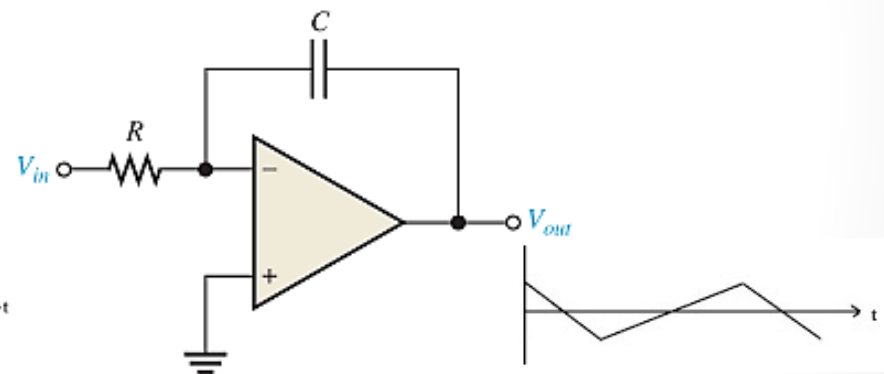

- Duty Cycle of the Astable Waveform indicates the rise and fall time of the sawtooth waveform i.e. positive or negative ramp.

# Sawtooth circuit...

## Astable Multivibrator & Integrator



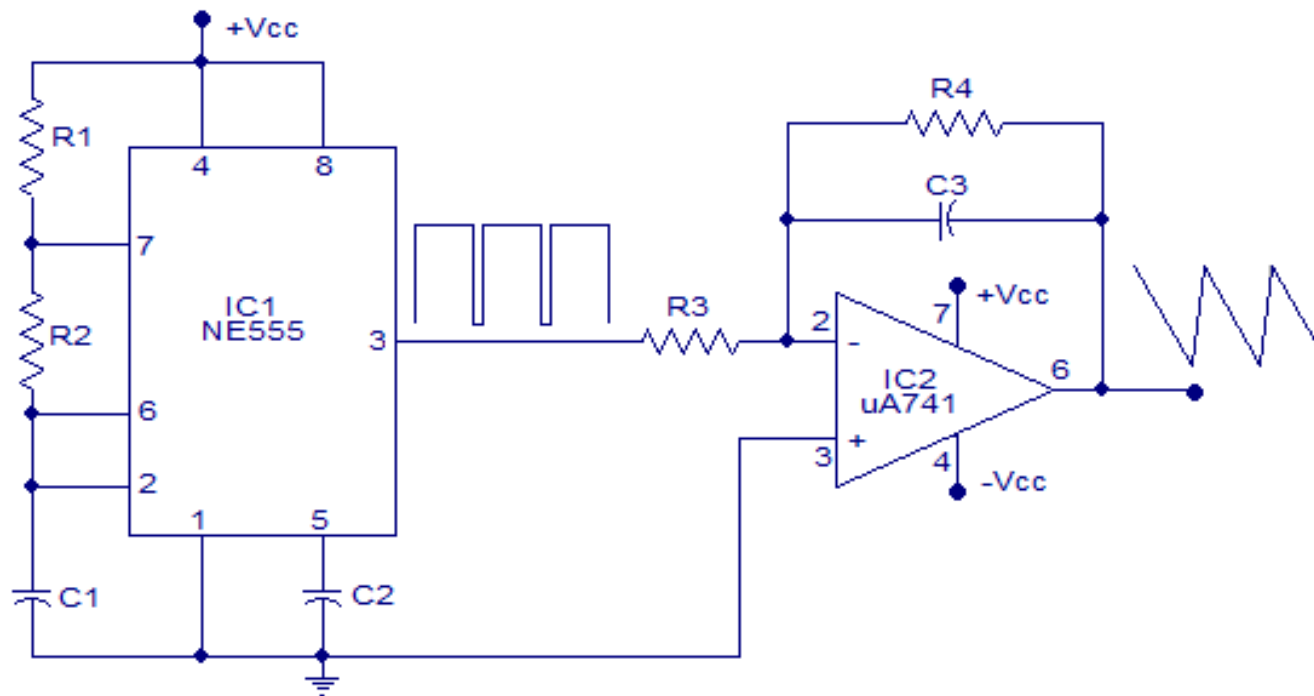


Sawtooth wave generator

[www.circuitstoday.com](http://www.circuitstoday.com)

# Sawtooth circuit....

Integrator & rapid discharge element

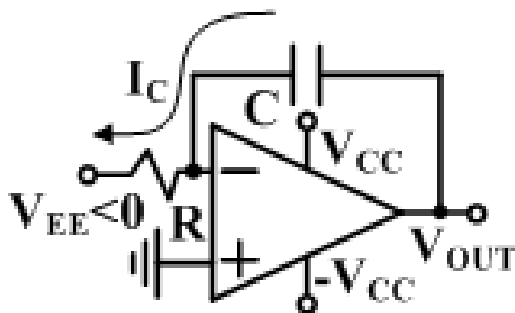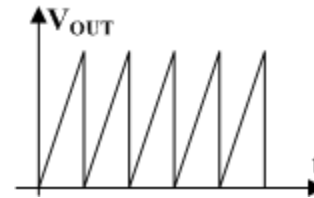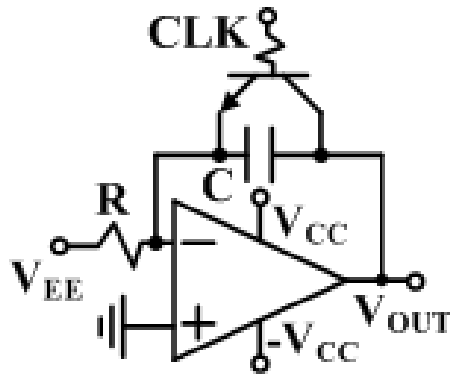



$$I_C = -\frac{V_{EE}}{R}$$

$$V_{OUT} = -\frac{V_{EE}}{RC}T = -\frac{V_{EE}}{RCf}$$


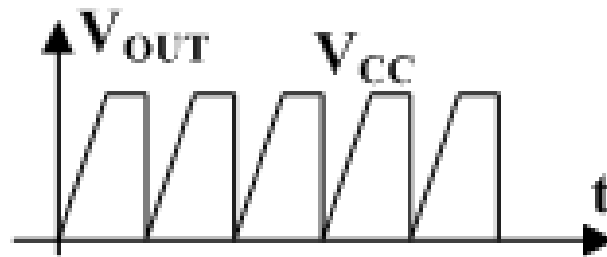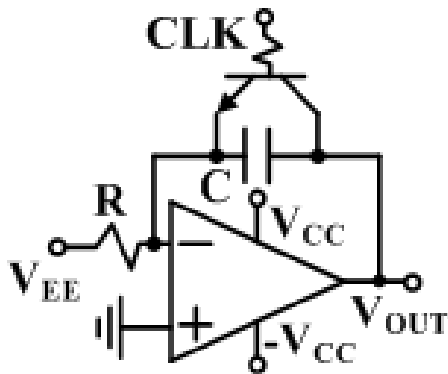
# Trapezoidal Generator circuit


If output voltage reaches  $V_{CC}$  during time  $T$ , op-amp sawtooth generator goes to saturation, and output voltage is **trapezoidal**.



# Sawtooth Voltage-Controlled Oscillator (VCO)

- VCO is a relaxation oscillator whose frequency can be changed by a variable dc control voltage.
- VCOs can be either sinusoidal or nonsinusoidal.
- One way to build a sawtooth VCO is with an op-amp integrator that uses a switching device (PUT) in parallel with the feedback capacitor to terminate each ramp at a prescribed level and effectively “reset” the circuit.
- The PUT is a programmable unijunction transistor with an anode, a cathode, and a gate terminal.

- Operation:

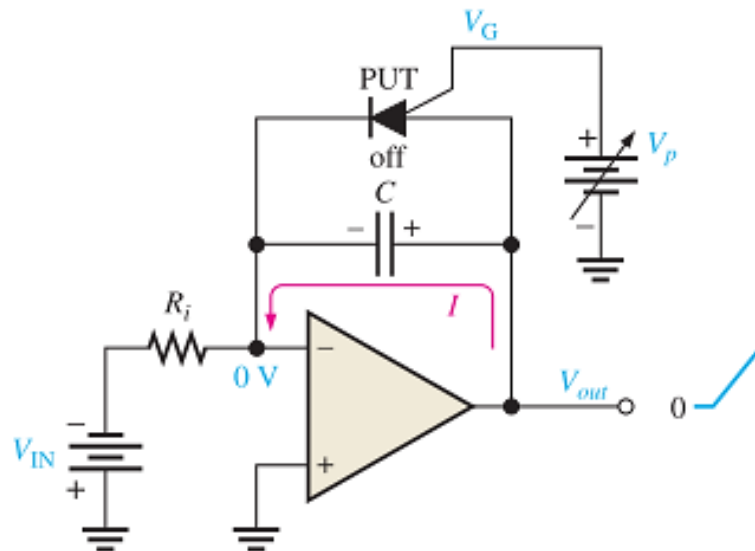


(a) Initially, the capacitor charges, the output ramp begins, and the PUT is off.

N.B.

For more details regarding PUT, refer to ch. 11

# Sawtooth VCO..

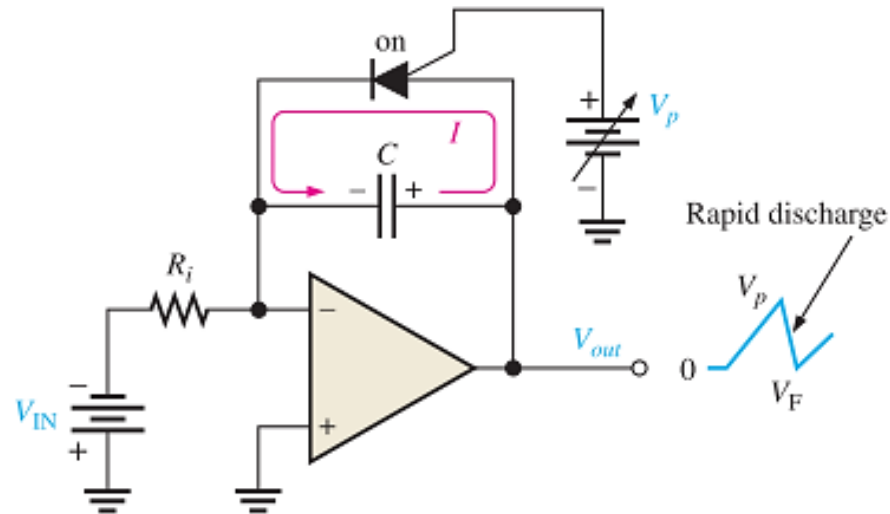

(b) The capacitor rapidly discharges when the PUT momentarily turns on.

T, of the sawtooth waveform: 
$$T = \frac{V_p - V_F}{|V_{IN}|/R_i C}$$

$f = 1/T$ , gives 
$$f = \frac{|V_{IN}|}{R_i C} \left( \frac{1}{V_p - V_F} \right)$$

# Assignment

- Design a sawtooth generator to provide a sawtooth waveform with the following specs:
  - frequency from 1 KHz to 1 MHz
  - amplitude from 0.5 Vpp to 6Vpp.

- For more details, refer to:
  - Chapter 16, T. Floyd, **Electronic Devices**, 9<sup>th</sup> edition.
  - Online tutorials on Sawtooth, Staircase generators.
- The lecture is available online at:
  - <http://bu.edu.eg/staff/ahmad.elbanna-courses/12884>
- For inquiries, send to:
  - [ahmad.elbanna@feng.bu.edu.eg](mailto:ahmad.elbanna@feng.bu.edu.eg)